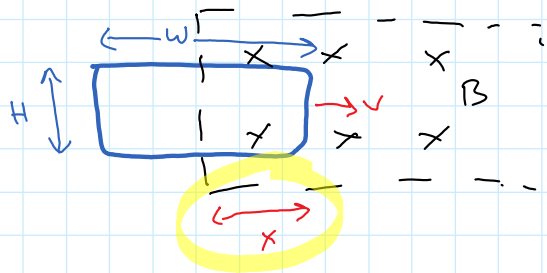


## Fingsh Ch 23

- Lenz's Law
- Inductors
- RL circuits
- Transformers

Worksheet  
p. 141



$$\Phi = BA$$

$$= BHx$$

$$\mathcal{E} = \frac{\Delta\Phi}{\Delta t} = \frac{\Delta(BHx)}{\Delta t}$$

$$= BH \frac{\Delta x}{\Delta t}$$

$$= BHv$$

	$\Phi$	$ \mathcal{E}  = \left  \frac{\Delta\Phi}{\Delta t} \right $
1	↑	same
2	↓	↓
3	same	same
4	↑	decreases to zero
5	same	↑
6	↑	↑
7	same	same (but opposite sign)
8	↑	↑

8	↑	↑
9	↑	Same

Worksheet  
p. 142

Find the  $\Phi_B$  for each case

$$\Phi_A = B \left( \frac{1}{4} WH \right)$$

$$\Phi_B = B \left( \frac{1}{2} WH \right)$$

$$\Phi_C = B \left( \frac{1}{2} WH \right)$$


$$\Phi_D = BHW$$

$$\Phi_E = BHW$$

$$\Phi_F = B \left( \frac{1}{2} HW \right)$$

$$\Phi_G = B \left( \frac{3}{4} HW \right)$$
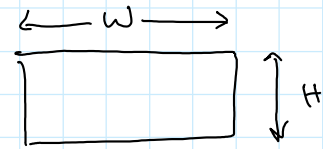
$$\Phi_H = B \left( \frac{1}{2} HW \right)$$



Now, find  $\mathcal{E}$  induced in each loop:

$$|\mathcal{E}_A| = BH \left( 2 \frac{cm}{s} \right)$$

$$\mathcal{E} = BHv$$

$$\mathcal{E}_B = 0 \quad \text{Nothing is changing}$$

$$\mathcal{E} = \frac{\Delta \Phi}{\Delta t} = \frac{\Delta (BHx)}{\Delta t}$$

$$|\mathcal{E}_C| = BH \left( 4 \frac{cm}{s} \right)$$

$$\mathcal{E}_D = 0$$

$$\mathcal{E}_E = 0$$



$$|\mathcal{E}_H| = BW \left( 2 \frac{cm}{s} \right)$$

$$|\mathcal{E}_F| = B W (2 \frac{cm}{s})$$

$$|\mathcal{E}_G| = B H (6 \frac{cm}{s})$$

$$|\mathcal{E}_H| = 0$$



### Inductance

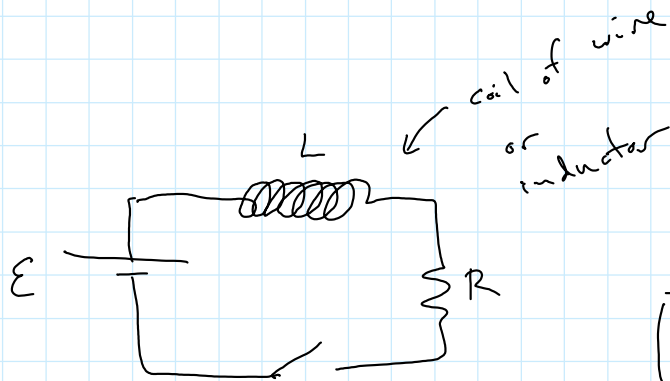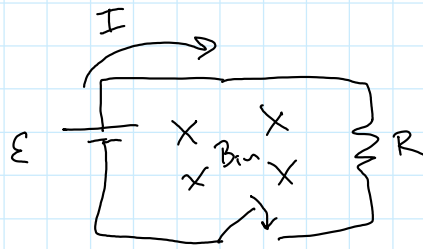

$$\mathcal{E}_L = N \frac{\Delta \Phi}{\Delta t} = L \frac{\Delta I}{\Delta t}$$

Since

$$L = N \left| \frac{\Delta \Phi}{\Delta I} \right|$$

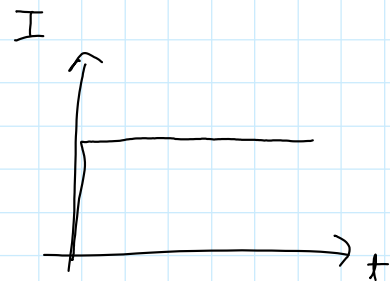
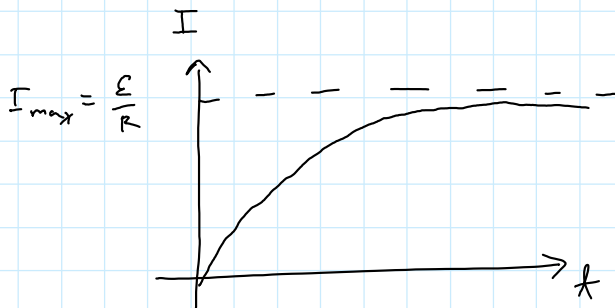


### RL circuit

$$I = \frac{\mathcal{E}}{R} \left( 1 - e^{-\frac{t}{\tau}} \right)$$

$$\tau = \frac{L}{R}$$

RC charging

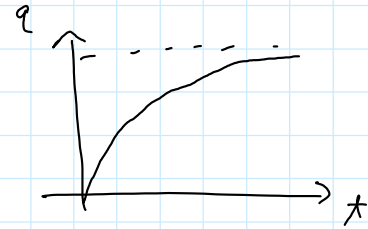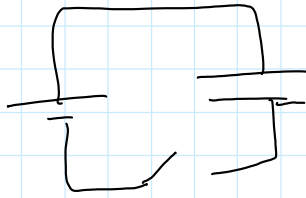


energy:

cap

$$U_c = \frac{1}{2} C V^2$$


inductor

$$U_L = \frac{1}{2} L I^2$$

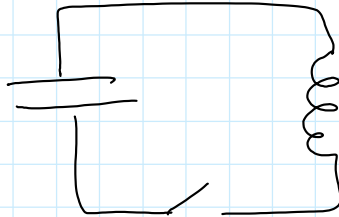


Applications

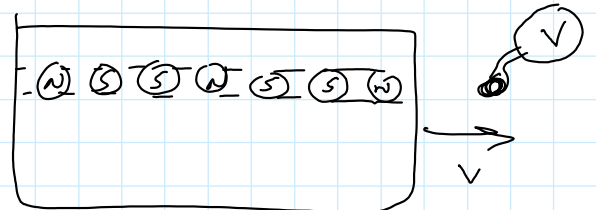- Credit Cards - Mag. stripe
- Speakers & mics
- Motors & generators
- Hybrid cars (back emf)



+ ↑ -

# Transformers

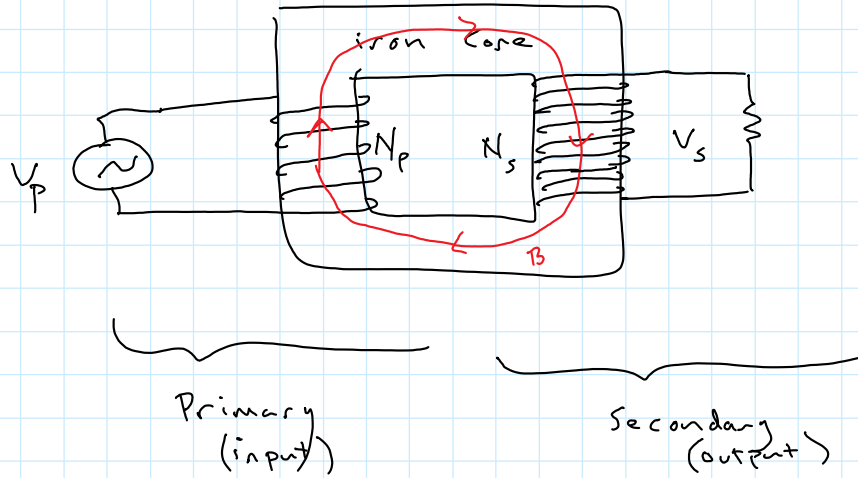

$V_s > V_p$       Step up transformer

$V_p > V_s$       Step down transformer


$P_p = P_s$       for ideal transformer

$I_p V_p = I_s V_s$


if  $V_s > V_p$       then  $I_s < I_p$





$$V_s = \frac{N_s}{N_p} V_p$$

$$I_s = \frac{N_p}{N_s} I_p$$

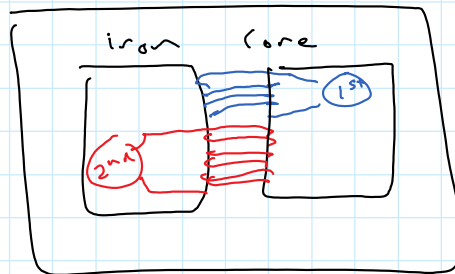


Transformer

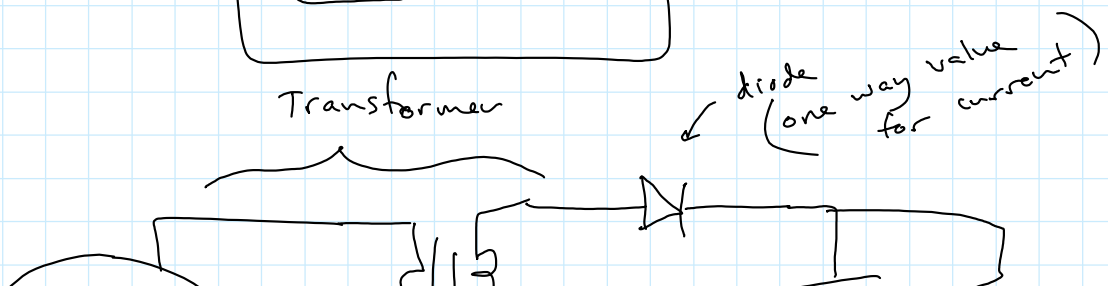


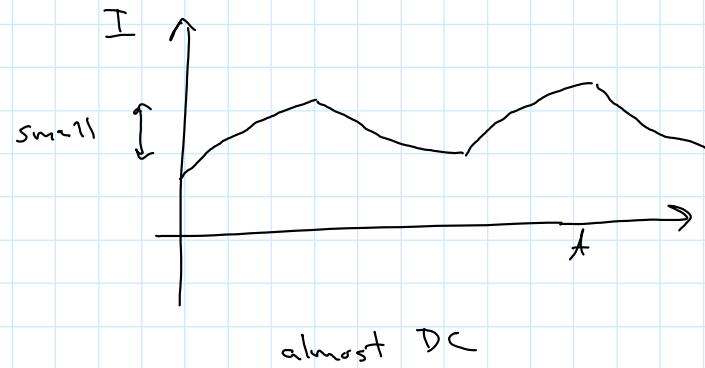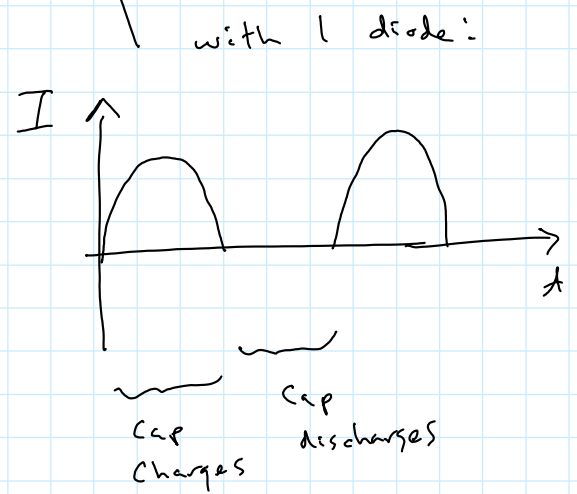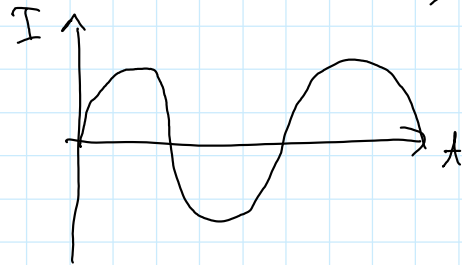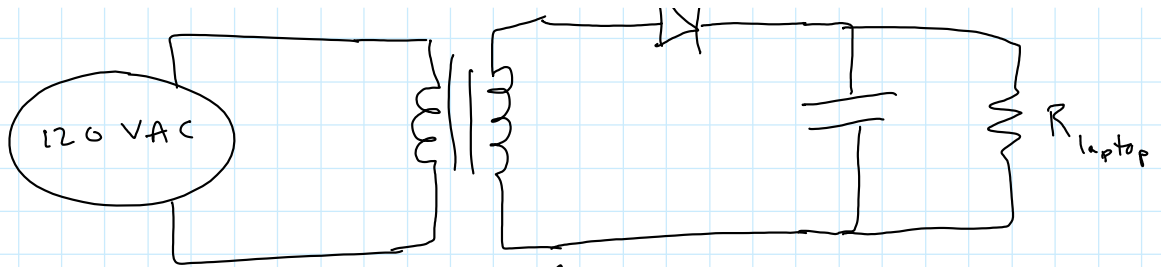


with 4 diodes:

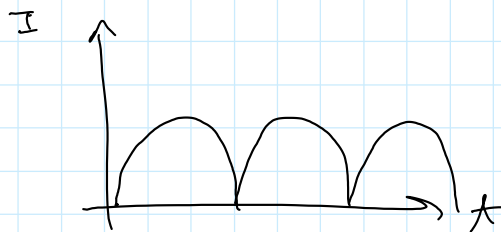

Prob 23-55

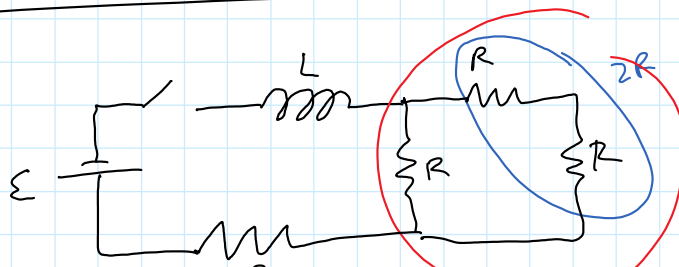
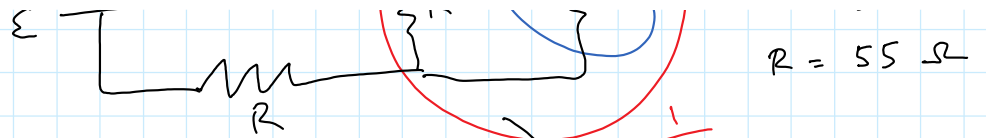
$$\begin{aligned} \epsilon &= 6 \text{ V} \\ L &= 37 \text{ mH} \\ R &= 55 \text{ } \Omega \end{aligned}$$



$$R = 55 \Omega$$


$$\tau = \frac{L}{R} = \frac{L}{R_{eq}}$$

find eq. circuit



I after a long time:

inductor has no effect on circuit:

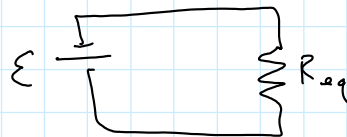

$$I_{max} = \frac{\epsilon}{R_{eq}}$$

$$I = I_{max} \left(1 - e^{-\frac{t}{\tau}}\right)$$

$$I \text{ at } t = 2\tau$$

$$I = \frac{\epsilon}{R_{eq}} \left(1 - e^{-\frac{2\tau}{\tau}}\right)$$

$$= \frac{\epsilon}{R_{eq}} \left(1 - \frac{1}{e^2}\right)$$

ch. 23-73

$$N_p = 25$$

$$N_s = 750$$

$$V_s = 4800 \text{ V}$$

$$I_s = 0.012 \text{ A}$$

$$V_p = \frac{N_p}{N_s} V_s = \frac{25}{750} (4800) = 160 \text{ V}$$

$$I_p = \frac{Z_s}{Z_p} I_s = \frac{750}{25} (6.012) = 0.36 \text{ A}$$