
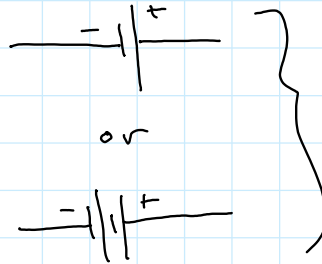


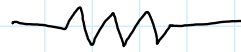
DC Circuits
Series + Parallel
Resistors
Capacitors




DC Power Supply
or
battery



Resistor

 

zero Resistance
path

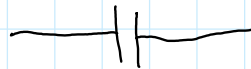

Worksheet
P. 23

- A) 1) Same in both
2) No
3) No



2 bulbs
in
series

- B) 1) more current
in single bulb

- 2) single bulb battery
has more current



single
bulb

- C) 1) increases total R
2) Total current decreases
as more resistors are added
in series


7.24

III


- A) 1) Same



III 71) 1) same

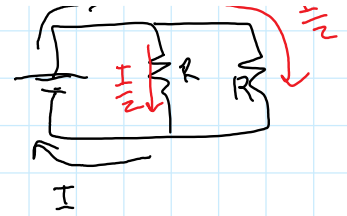

2)

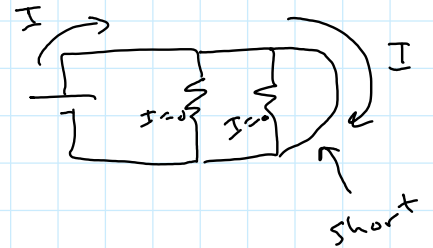

B) about the same

current through battery for single bulb is half that of 2 bulb circuit

C) current through battery increase with more bulbs in parallel

D) yes

E) No

Application of the def:
Saw stop


current

$$I = \frac{\Delta Q}{\Delta t}$$




units:

A ampere
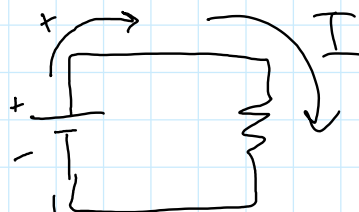
$$1 \text{ A} = \frac{1 \text{ C}}{1 \text{ s}}$$




batteries:

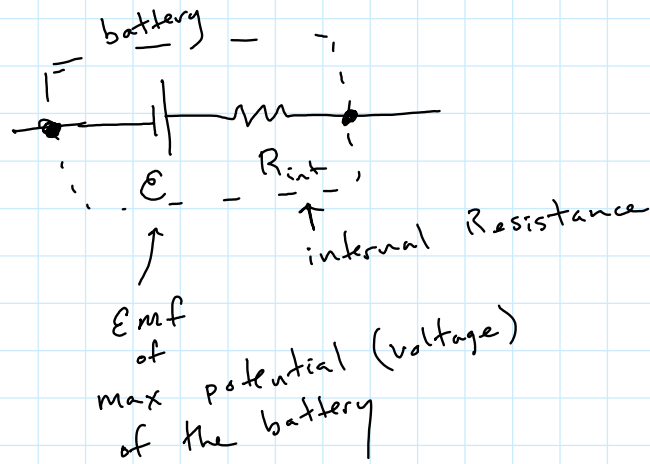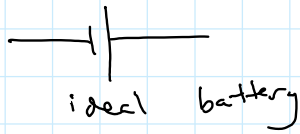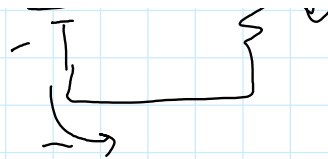

Resistance and Ohm's Law

Ohm's Law: $\Delta V = I R$

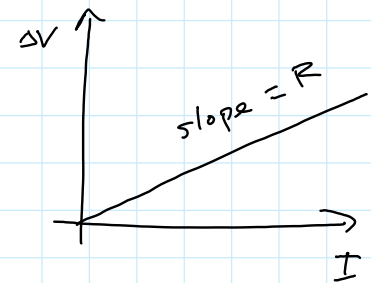

Resistance:



worksheet
p. 325

Top





a) increases

b) increases

- b) increases
- c) decreases
- d) (iv) don't know


bottom same current

Which charges move?

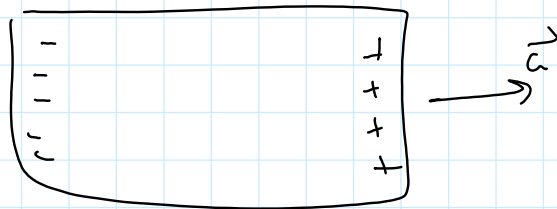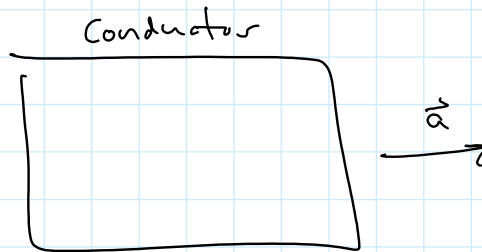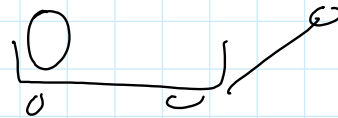
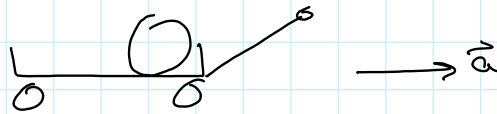


Negative charges move

Series & Parallel Resistors


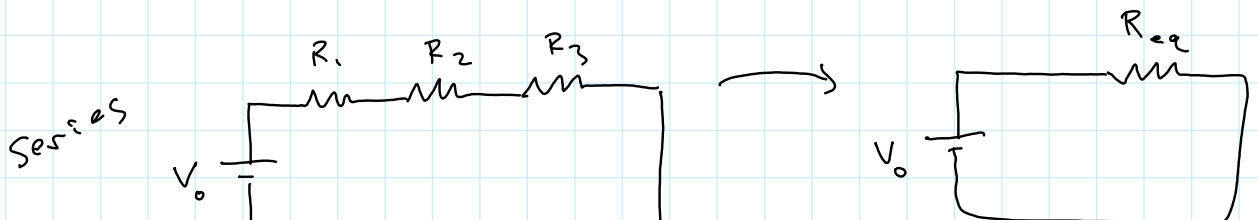


Series

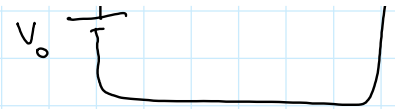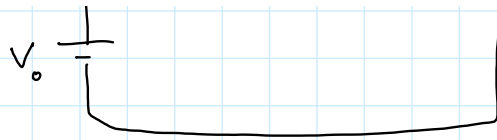

$$R_{eq} = R_1 + R_2 + R_3 + \dots$$

Parallel

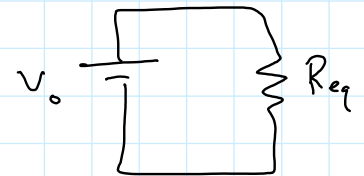
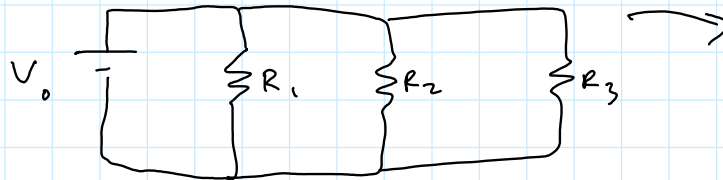


$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

P325

bottom

Find I if $V = 12V$

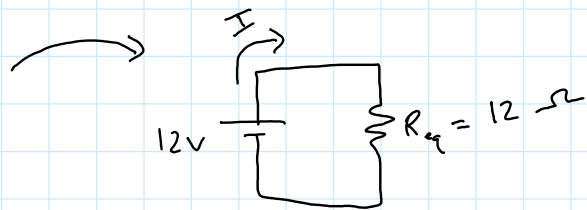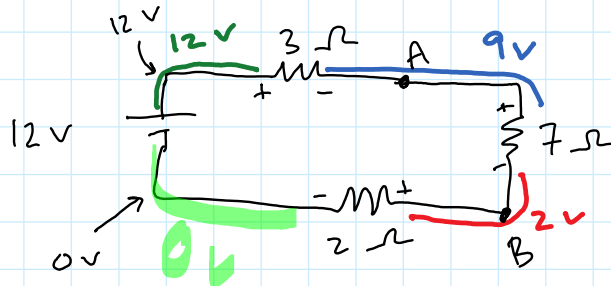

$$\begin{aligned} \frac{3\Omega}{V} &= IR \\ &= (1A)(3\Omega) \\ &= 3V \end{aligned}$$

$$\begin{aligned} \frac{7\Omega}{V} &= IR \\ &= (1)(7) \\ &= 7V \end{aligned}$$

$$\begin{aligned} V &= IR \\ (12V) &= I(12\Omega) \\ I &= 1A \end{aligned}$$


worksheet
-24

b)		ΔV	I
----	--	------------	-----

Worksheet
12.324

b)

	ΔV	I	R
Battery	12 V	4 A	
R_1	8 V	4 A	2 Ω
R_2	4 V	4 A	1 Ω

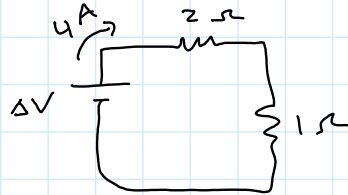

$$V = IR$$

a)

	ΔV	I	R
Battery	15	8 A	
R_1	15	3 A	5 Ω
R_2	15	5 A	3 Ω