
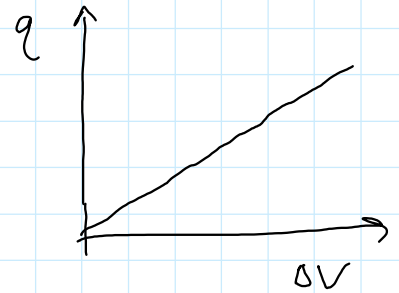


Exam #2 → Wed 2/4

DC Circuits
Series + parallel
Resistors + Capacitors

Capacitors

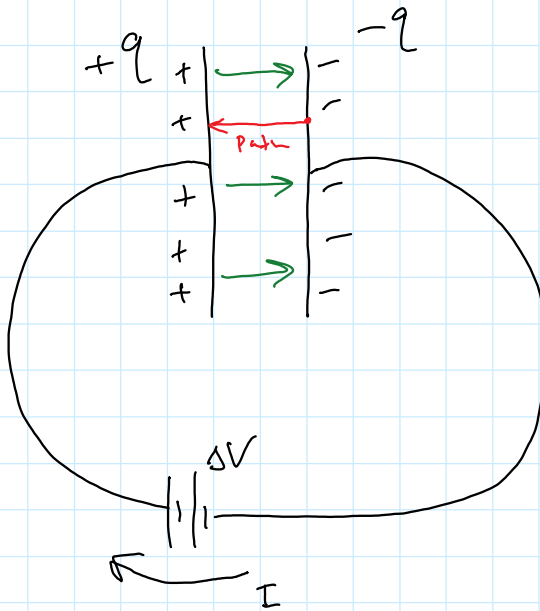


$$Q = C V$$


↑
Capacitance


depends on
physical properties
→ size of plates
→ spacing between plates

Types of Capacitors:

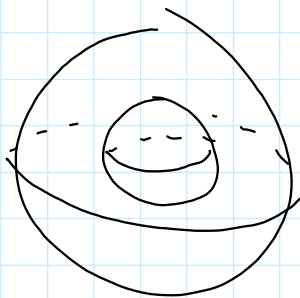

Spherical Capacitor

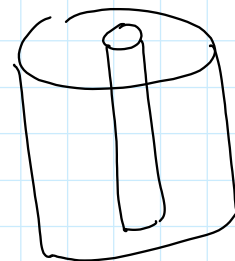

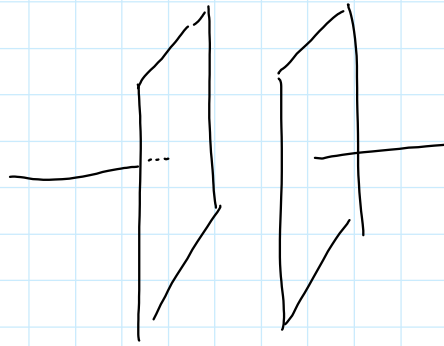




← most common

parallel plate capacitor

Parallel plate capacitor

$$C = \frac{A \epsilon_0}{d}$$

Dielectric

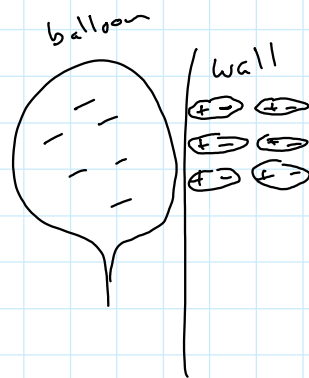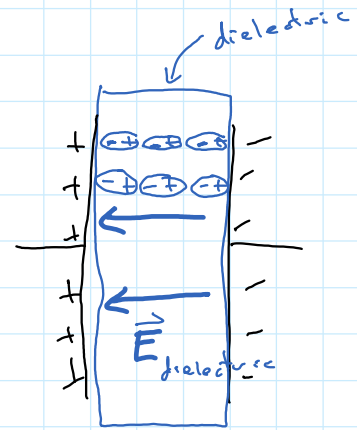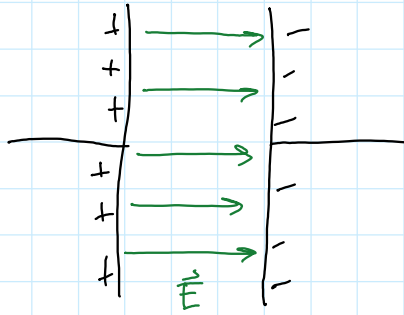

$$C = K C_0$$

↑
dielectric constant

$$K \geq 1$$

corr
 $k = 1$


Worksheet
 p. 85

- | | |
|---------|----------|
| 1) ↓ | 7) ↓ |
| 2) ↑ | 8) ↑ |
| 3) same | 9) same |
| 4) ↑ | 10) ↑ |
| 5) same | 11) ↑ |
| 6) same | 12) same |

$Q = CV$

Series and Parallel Capacitors


parallel

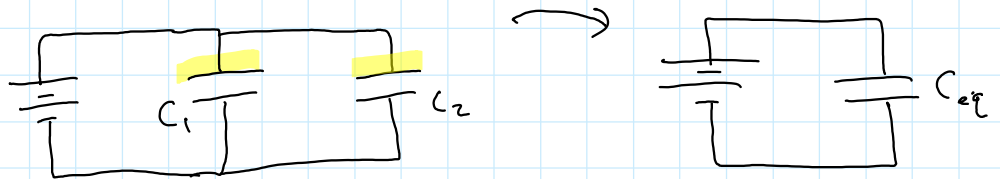

$C_{eq} = C_1 + C_2 + \dots$

parallel

series

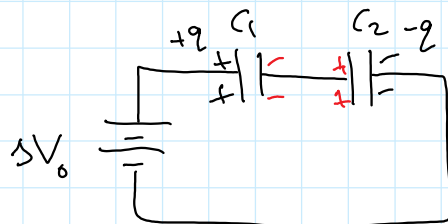

$q = CV$


$q_1 = q_2$

$\Delta V_1 + \Delta V_2 = \Delta V_0$

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots$$

series

	Resistor	Capacitor
Series	$I \text{ same } I_1 = I_2 = I_3 \dots$ $\Delta V_{total} = \Delta V_1 + \Delta V_2 + \dots$	$Q_{total} = Q_1 = Q_2 = Q_3 \dots$ $\Delta V_{total} = \Delta V_1 + \Delta V_2 + \Delta V_3 + \dots$
Parallel	$I_{total} = I_1 + I_2 + I_3 \dots$ $\Delta V_{total} = \Delta V_1 = \Delta V_2 = \Delta V_3 \dots$	$Q_{total} = Q_1 + Q_2 + Q_3 + \dots$ $\Delta V_{total} = \Delta V_1 = \Delta V_2 = \Delta V_3 \dots$

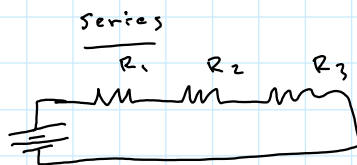

Application of the Day:

Capacitors: store charge or energy

Flash on cameras

Defibrillators

Super Capacitors or Ultra Cap. → like a battery


work sheet

1) Find C_{eq} for each circuit

Worksheet
1.89

- 1) Find C_{eq} for each circuit
- 2) if $V_{battery} = 12V$
find q on each capacitor
- 3) find ΔV for each capacitor

Series

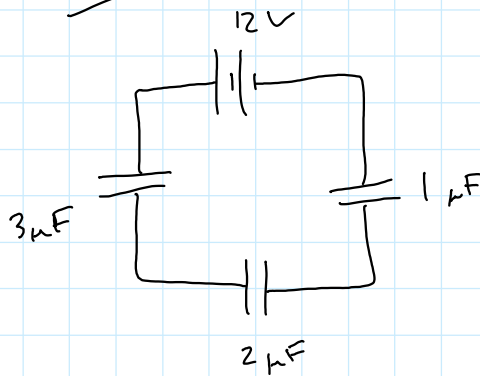

Parallel



$$\begin{aligned}\frac{1}{C_{eq}} &= \frac{1}{3} + \frac{1}{2} + \frac{1}{1} \\ &= \frac{2}{6} + \frac{3}{6} + \frac{6}{6} \\ &= \frac{11}{6}\end{aligned}$$

$$C_{eq} = \frac{6}{11} \mu F$$

$$\begin{aligned}Q_{total} &= C_{eq} \Delta V_{battery} \\ &= \left(\frac{6}{11} \mu F\right) (12V) \\ &= \frac{72}{11} \mu C\end{aligned}$$

$$Q_A = Q_B = Q_C = Q_{total} = \frac{72}{11} \mu C$$

$$\begin{aligned}C_{eq} &= 3 + 2 + 1 \\ &= 6 \mu F\end{aligned}$$

$$\begin{aligned}Q_{total} &= C_{eq} \Delta V_{battery} \\ &= (6 \mu F)(12V) \\ &= 72 \mu C\end{aligned}$$

$$Q_A = C_A V_A$$

$$Q_A = Q_B = Q_C = Q_{\text{total}} = \frac{72}{11} \mu\text{C}$$

$$Q_A = C_A V_A \\ = (3 \mu\text{F})(12 \text{V}) \\ = 36 \mu\text{C}$$

$$Q_A = C_A V_A \\ V_A = \frac{Q_A}{C_A} = \frac{\frac{72}{11}}{3} = \frac{24}{11} \text{V}$$

$$Q_B = C_B V_B \\ = (2 \mu\text{F})(12 \text{V}) \\ = 24 \mu\text{C}$$


$$V_B = \frac{Q_B}{C_B} = \frac{\frac{72}{11}}{2} = \frac{36}{11} \text{V}$$

$$Q_C = 12 \mu\text{C}$$

$$V_C = \frac{Q_C}{C_C} = \frac{\frac{72}{11}}{1} = \frac{72}{11} \text{V}$$

$$Q_{\text{total}} = Q_A + Q_B + Q_C = 72 \mu\text{C}$$

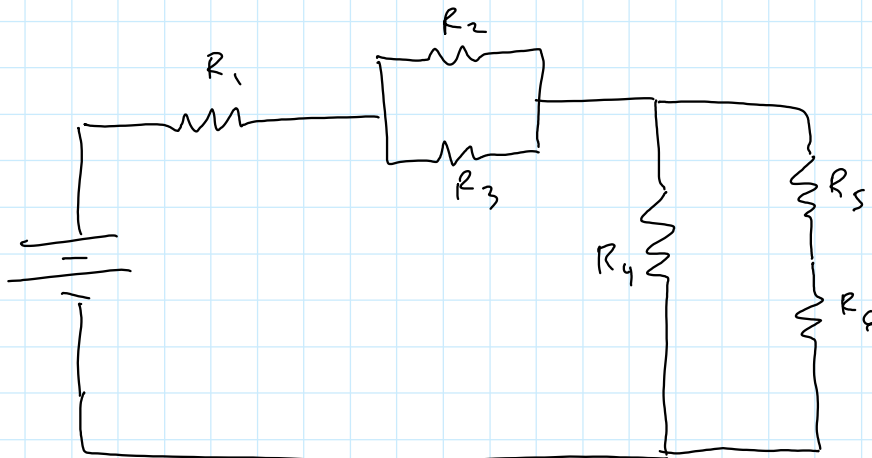
$$V_A + V_B + V_C = 12 \text{V} \quad \checkmark$$



Kirchhoff's Rules

Junction Rule :

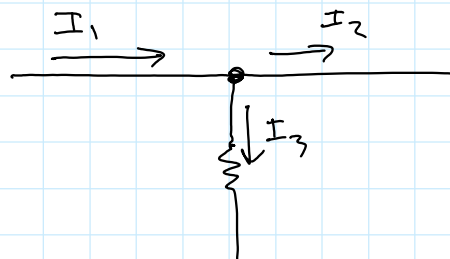
$$\sum I_{\text{in}} = \sum I_{\text{out}}$$





$$I_1 = I_2 + I_3$$

Loop Rule:

$$\sum_{\text{Loop}} \Delta V = 0$$

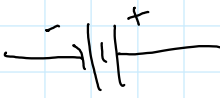battery: 

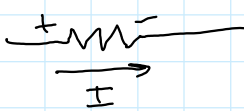Resistor: 

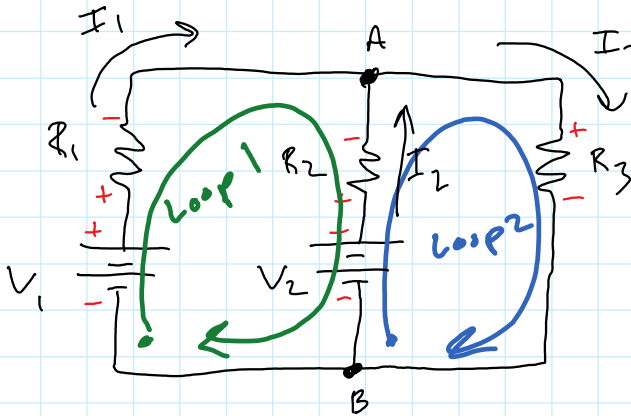

- 1) Assign direction to current in each branch (guess)
- 2) Indicate the high/low potentials with +/- signs for each device
- 3) Apply Junction Rule
- 4) Apply 2 loop Rules

Junction: $\sum I_{in} = \sum I_{out}$

$$I_1 + I_2 = I_3$$

Loop 1: $+V_1 - I_1 R_1 + I_2 R_2 - V_2 = 0$

Loop 2:

$$+V_2 - I_2 R_2 - I_3 R_3 = 0$$

Solve for I_1 , I_2 , and I_3