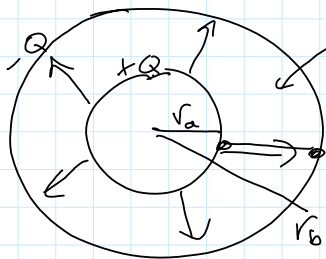


Goals for the Lecture:

- 1) Be able to calculate the capacitance of a capacitor from Gauss's Law and the definition of capacitance ($Q=CV$)
- 2) Be able to find equivalent capacitance of capacitors in series and parallel circuits
- 3) Be able to calculate the energy stored in a capacitor

Find C : Two concentric spherical conductors



$$E = \frac{kQ}{r^2}$$

$$\Delta V = - \int \vec{E} \cdot d\vec{s}$$

$$\Delta V = - \int_{r_a}^{r_b} \frac{kQ}{r^2} dr \cos 0^\circ$$

$$= kQ \left[+\frac{1}{r} \Big|_{r_a}^{r_b} \right]$$

$$|\Delta V| = \left| kQ \left(\frac{1}{r_b} - \frac{1}{r_a} \right) \right|$$

$$\Delta V = kQ \left(\frac{1}{r_a} - \frac{1}{r_b} \right)$$


for a capacitor: $Q = C \Delta V$

$$Q = \frac{1}{k \left(\frac{1}{r_a} - \frac{1}{r_b} \right)} \Delta V$$


$$C = \frac{1}{k \left(\frac{1}{r_a} - \frac{1}{r_b} \right)} \quad \text{for a spherical capacitor}$$

Combinations of Capacitors:




Series:

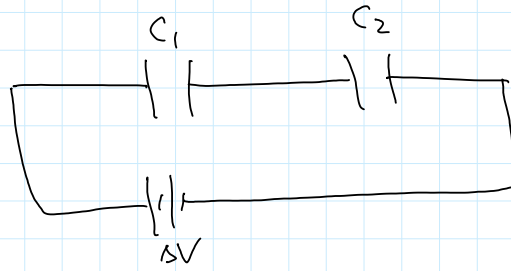


Parallel:

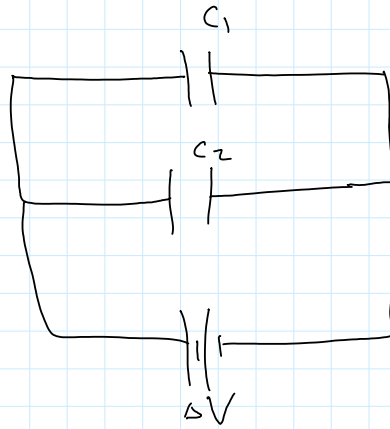

Circuits:

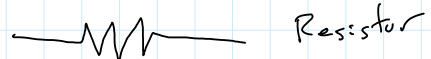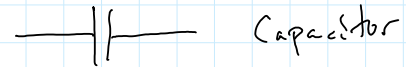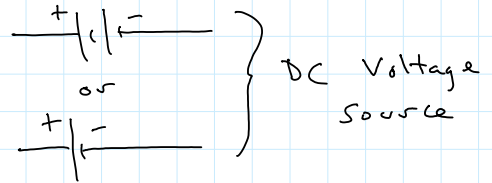

Parallel

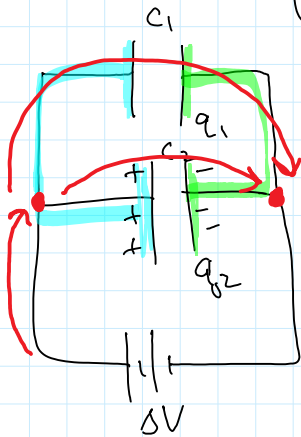


In Parallel:


$$C_{eq} = C_1 + C_2 + \dots$$

Voltage is same on every Cap. in parallel

Series

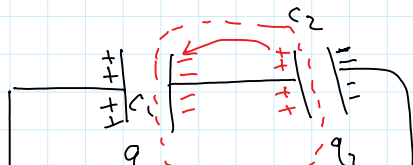

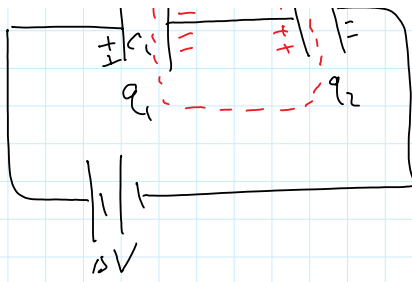Charge on every Cap. in series
 $q_1 = q_2 = \dots$
 is the same



$q_1 = q_2$
is the same

In Series:

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots$$

$$Q = CV$$



$$q_1 = C_1 V_1$$

$$q_2 = C_2 V_2$$

$$q_1 = q_2 = q$$


$$\Delta V = V_1 + V_2$$

$$\Delta V = \frac{q}{C_1} + \frac{q}{C_2}$$

$$\Delta V = \left(\frac{1}{C_1} + \frac{1}{C_2} \right) q$$


$$\left(\frac{1}{\frac{1}{C_1} + \frac{1}{C_2}} \right) \Delta V = q$$


↑
 C_{eq}

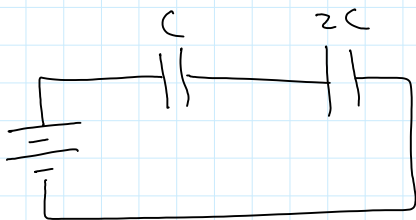


$$\frac{1}{C_{eq}} = \frac{1}{C} + \frac{1}{2C} = \frac{3}{2C}$$

$$C_{eq} = \frac{2C}{3}$$

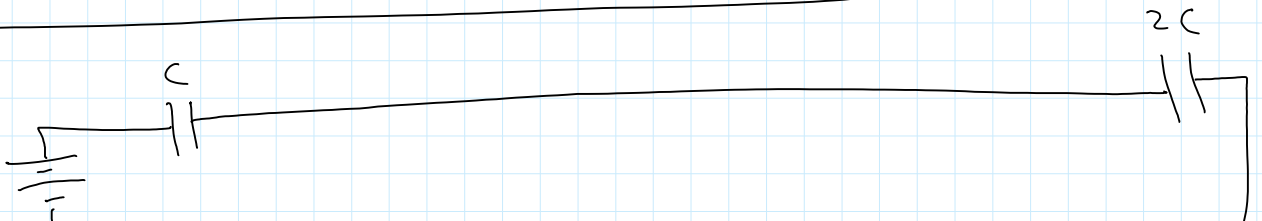

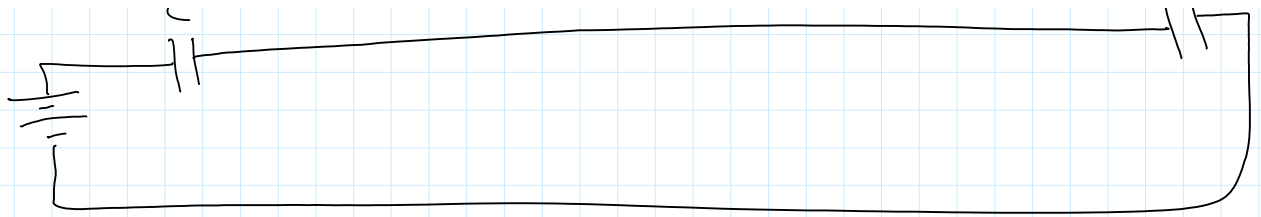


$$C_{eq} = \frac{2}{3} C$$

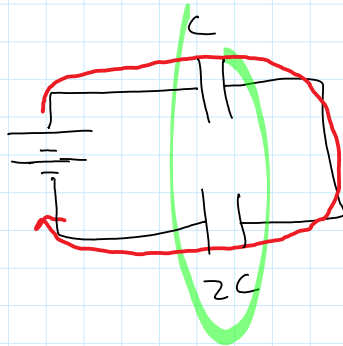


In Series

$$C_{eq} = \frac{2}{3} C$$

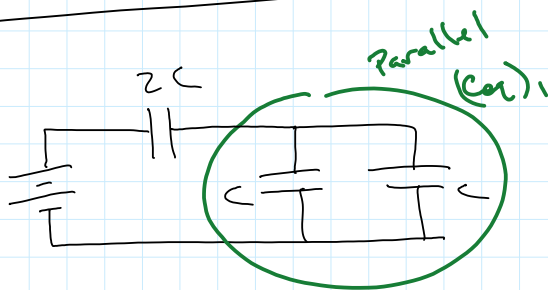



$$(C_{eq})_1 = C + C = 2C$$

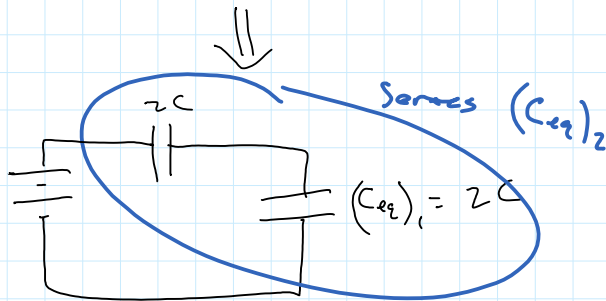

$$\frac{1}{(C_{eq})_2} = \frac{1}{2C} + \frac{1}{(C_{eq})_1} = \frac{2}{2C}$$


$$(C_{eq})_2 = C$$

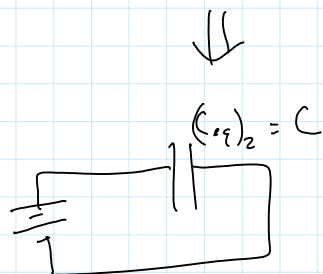




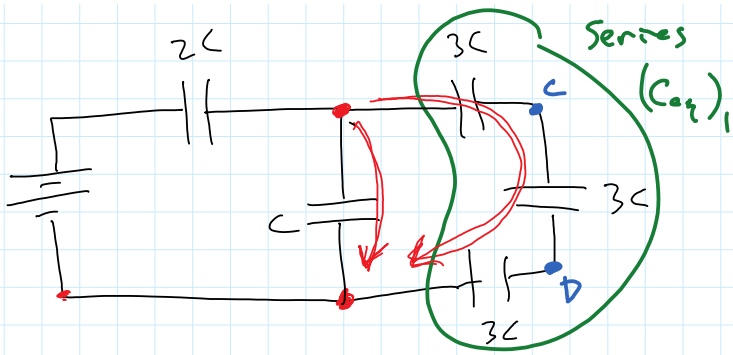


$$\frac{1}{(C_{eq})_1} = \frac{1}{3C} + \frac{1}{3C} + \frac{1}{3C} = \frac{3}{3C}$$

$$(C_{eq})_1 = C$$

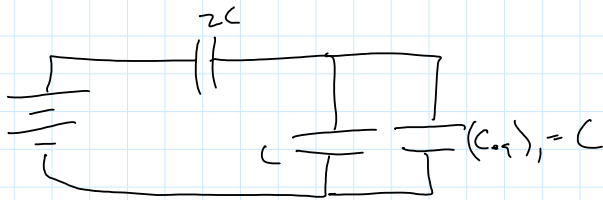

Like above

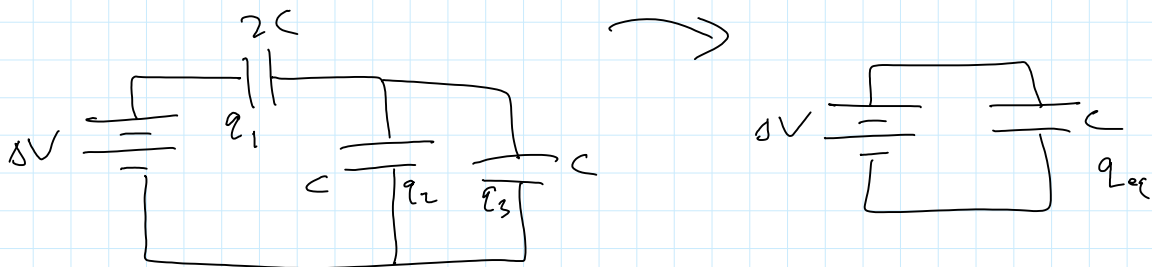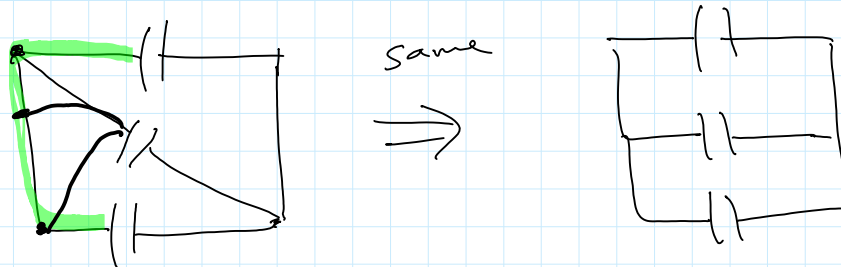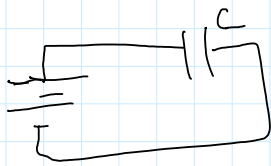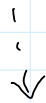

$$\text{let } C = 1 \text{ F}$$
$$\Delta V = 6 \text{ V}$$

$$q_{\text{eq}} = C_{\text{eq}} V$$
$$= (1 \text{ F})(6 \text{ V})$$
$$= 6 \text{ C}$$

work backwards

