

Capacitors:


Electric Potential Energy:

$$U = \frac{Q^2}{2C} = \frac{1}{2} Q \Delta V = \frac{1}{2} C (\Delta V)^2$$


for any capacitor

since $Q = C \Delta V$

Dielectrics - electrical insulator

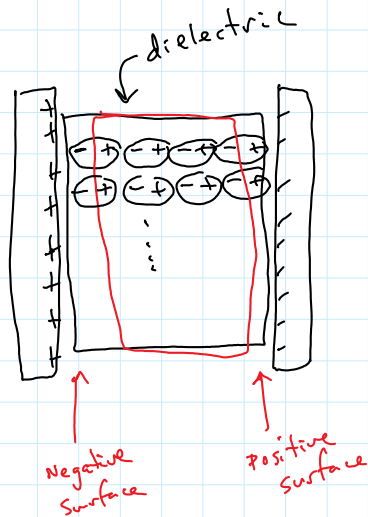

Let's look at the \vec{E} fields:

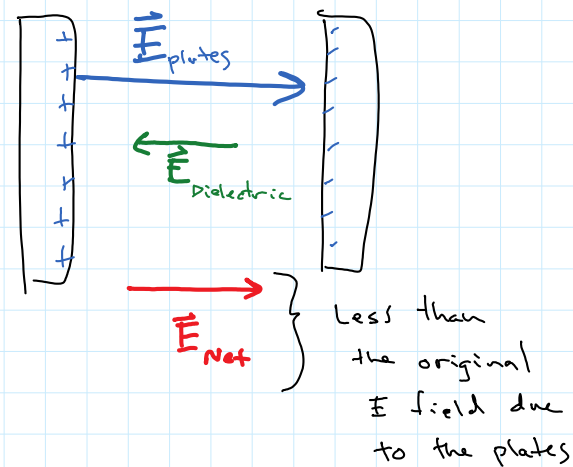

for parallel plate capacitor:

$$C = k \frac{\epsilon_0 A}{d}$$

k = Dielectric constant

$$k \geq 1$$


in general:

$$C = k C_0$$


C_0 ← Capacitance without dielectric
 k ← Dielectric constant

Capacitance with dielectric completely filling volume between plates

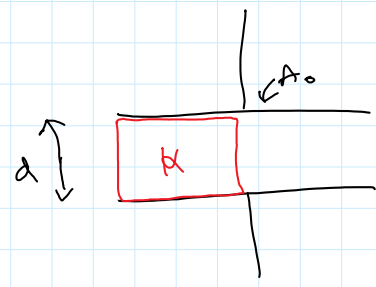Parallel Plate: $C = \frac{\kappa \epsilon_0 A}{d}$



Like 2 Capacitors in parallel

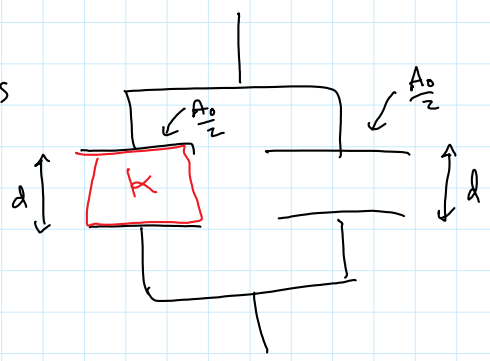

original capacitance with No dielectric is $C_0 = \frac{\epsilon_0 A_0}{d}$


Let $C_1 =$ capacitance of left cap.
 $C_2 =$ " " " Right cap

$$C_1 = \frac{\kappa \epsilon_0 \frac{A_0}{2}}{d} \quad C_2 = \frac{\epsilon_0 \frac{A_0}{2}}{d}$$


$$C = C_1 + C_2 \quad \text{Parallel}$$

$$= \kappa \frac{C_0}{2} + \frac{C_0}{2}$$

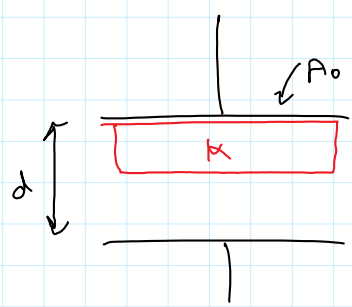
$$= \left(\frac{\kappa + 1}{2} \right) C_0$$






Like 2 in series

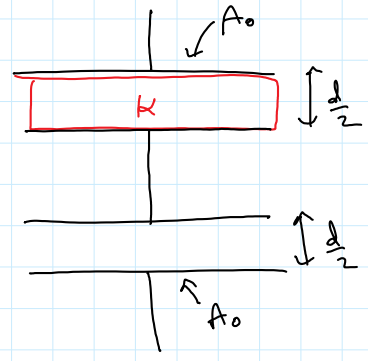


Current: moving charges

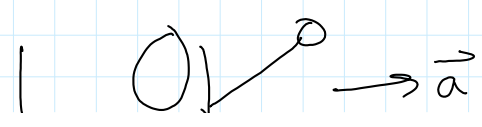

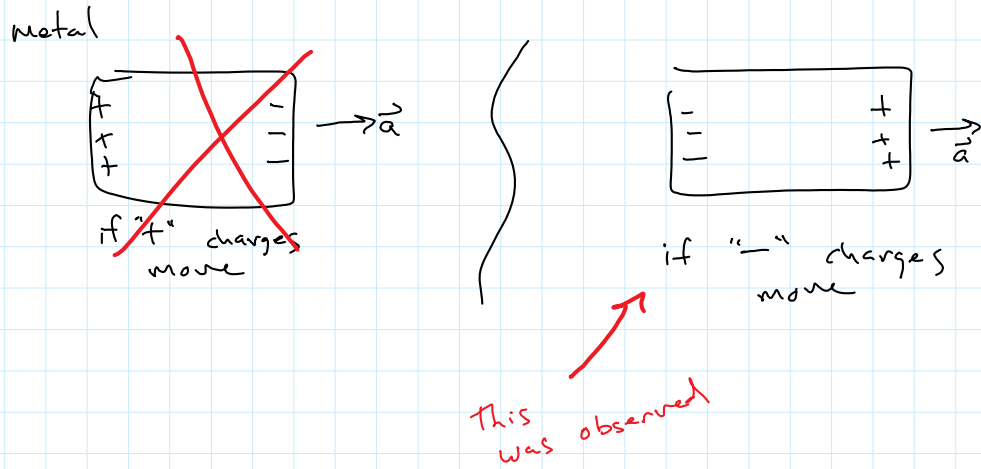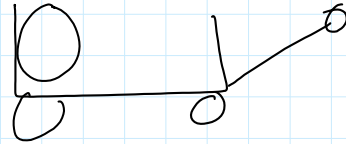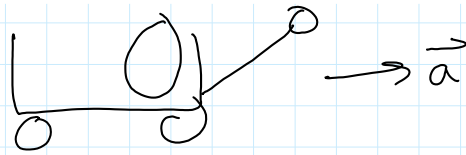

Conductive material

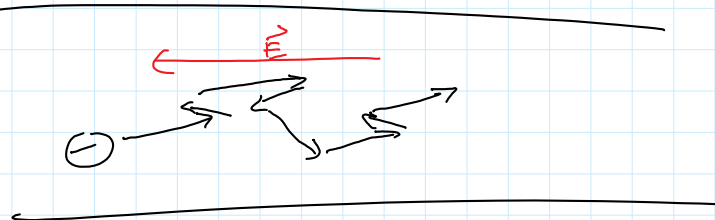

overall or average motion is opposite \vec{E} at \vec{v}_{drift}

Worksheet
p. 101

A) Same
same current

B) 1) $R_x < R_y$

2) same

3) same

- 1) V_{bat}
 3) same

$$P = I V = I^2 R = \frac{V^2}{R}$$

$$V = IR$$

c) $B_2 > B_1 > B_3$

Resistor:

$$V = IR \quad \text{ohm's Law}$$

P. 102 A) same $V_{\text{bat}} = V_{\text{bulb}} = 3.2 \text{ V}$

B) $I_1 = I_2 = \frac{I_{\text{single}}}{2}$ $V_{\text{bat}} = 3.6 \text{ V}$
 $V_1 = V_2 = 1.8 \text{ V}$

1) $(V_{\text{bat}})_1 = (V_{\text{bat}})_2$

2) $V_{\text{single}} \rightarrow V_1 = V_2$

c) same as V_{battery}

P. 103 D) $I_1 = I_2$
 $I_1 + I_2 = I_{\text{battery}}$

1) $V_{\text{bat}} = V_1 = V_2 = V_{\text{single}}$

3) same

E) 1) yes

2) NO \rightarrow constant ΔV

A)

$$\begin{array}{ccccc} V_{\text{battery}} & > & V_1 & > & V_2 = V_3 \\ \uparrow & & \uparrow & & \uparrow \\ 7.7 \text{ V} & & 5.9 \text{ V} & & 1.7 \text{ V} \\ \downarrow & & \underbrace{\hspace{2cm}} & & \\ 7.7 & \approx & 7.6 \text{ V} & & \end{array}$$

P. 104

B)

$$I_{\text{battery}} > I_1 > I_2 = I_3$$

$$V_{\text{battery}} = V_1 > V_2 = V_3$$
$$V_1 = 2V_2$$

C)

