

Current and resistance:
direction of positive charge flow



$$I = \frac{dQ}{dt}$$

units: $\frac{C}{s} = A$
↑
ampere


$$R = \rho \frac{l}{A}$$

↑
resistivity
of the
material

$$R = R_0 [1 + \alpha (T - T_0)]$$

↑
resistance
at T_0


↑
temp.
coefficient
of
resistivity

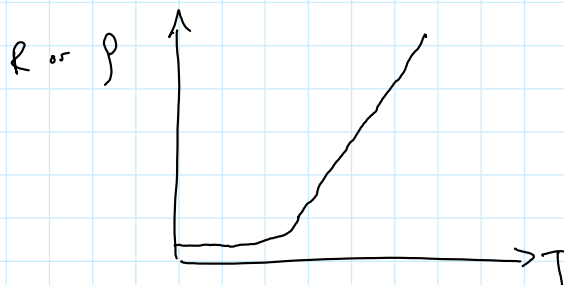

Superconductors



Superc

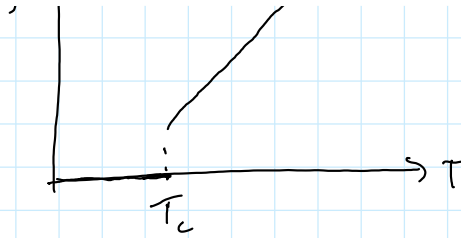

Power :

$$P = \frac{\text{energy}}{\text{time}}$$


units $\frac{J}{s} = W$
 \uparrow
 watt

$$P = \begin{cases} I V \\ I^2 R \\ \frac{V^2}{R} \end{cases}$$

Since $V = IR$

Resistors:

Series

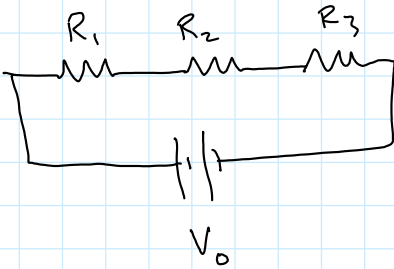


$$\Delta V_1 + \Delta V_2 + \Delta V_3 = \Delta V_0$$

$$I_1 = I_2 = I_3 = I_{\text{battery}}$$

$$R_{eq} = R_1 + R_2 + R_3 + \dots$$

Parallel


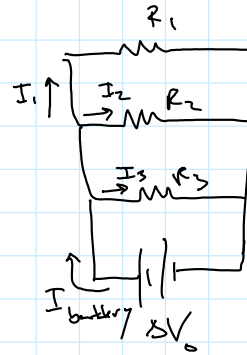


$$\Delta V_1 = \Delta V_2 = \Delta V_3 = \Delta V_0$$



$$I_1 + I_2 + I_3 = I_{\text{battery}}$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$


Fund Req:

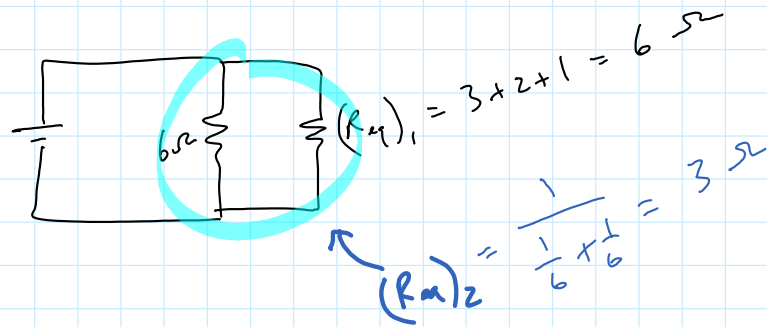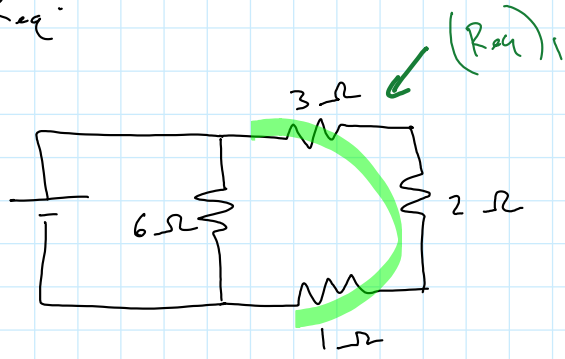

\Downarrow

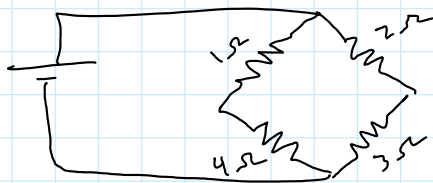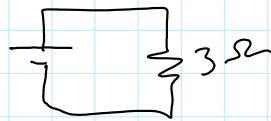



\Rightarrow

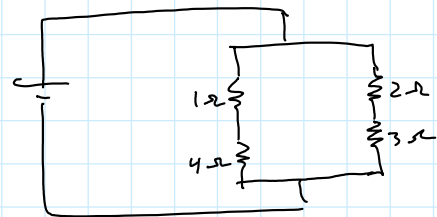

\Downarrow




\Downarrow

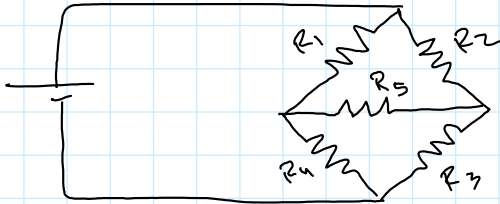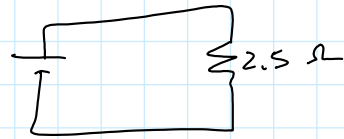

- $R_1 = 1 \Omega$
- $R_2 = 2 \Omega$
- $R_3 = 3 \Omega$
- $R_4 = 5 \Omega$
- $R_5 = 5 \Omega$

We need Kirchhoff's Rules

Kirchhoff's Rules:

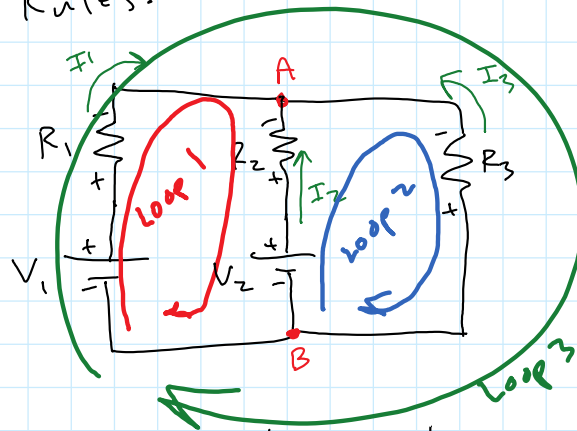

given: R_1, R_2, R_3
 V_1 and V_2

Find: I_1, I_2, I_3

1) Define the current direction in each branch (just guess)

2) Junction Rule: $\sum I_{in} = \sum I_{out}$

at junction A: $\sum I_{in} = \sum I_{out}$

$$I_1 + I_2 + I_3 = 0$$

at junction B:



$$0 = I_1 + I_2 + I_3$$

same as junction A

No New information

3) Mark high voltage side of each device with "+"
" Low " " " " " " " "

" Low " " " " " " " " " " " "

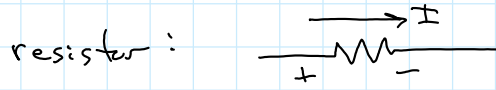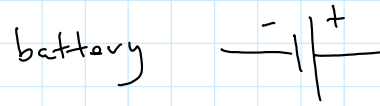

I flows from high to low potential

4) Loop Rule: $\sum \Delta V_{loop} = 0$

Loop 1: $+V_1 - I_1 R_1 + I_2 R_2 - V_2 = 0$

Loop 2: $+V_2 - I_2 R_2 + I_3 R_3 = 0$

3 equations \rightarrow solve for 3 unknowns

Let $R_1 = 0.01 \Omega$

$R_2 = 1 \Omega$

$R_3 = 0.06 \Omega$

$V_1 = 12 \text{ V}$

$V_2 = 10 \text{ V}$

$I_3 = -171 \text{ A}$

$I_2 = -0.283 \text{ A}$

To solve for I_1 :


$I_1 + I_2 + I_3 = 0$


$I_1 + (-0.283) + (-171) = 0$

$I_1 = +171.283 \text{ A}$

Keep the Negative sign until you have finished solving for everything

Actual Flow of current:

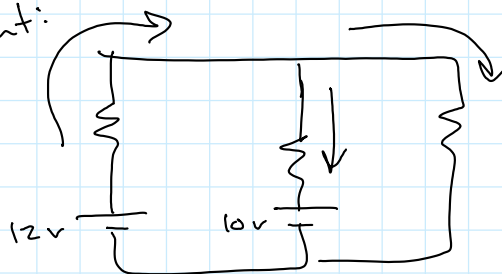

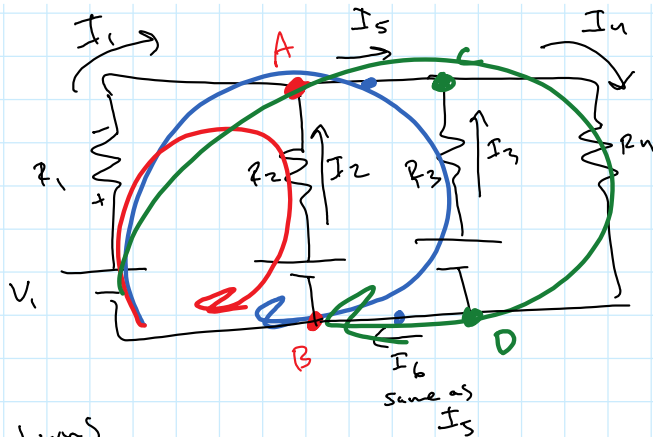

Junctions

$$A: I_1 + I_2 = I_5 \quad \left. \vphantom{A} \right\} I_5 = I_6$$

$$B: I_6 = I_1 + I_2$$

Junction A + B are the same

$$C: I_3 + I_5 = I_4$$

$$D: I_4 = I_3 + I_5$$

Junction C + D are the same

2 junction rules:

$$\begin{cases} I_3 + I_5 = I_4 \\ I_1 + I_2 = I_5 \end{cases}$$


5 equations to solve for 5 unknowns


3 Loops

Problem:


given: $R_1, R_2, R_3, V_1, V_2, V_3$

find: I_1, I_2, I_3

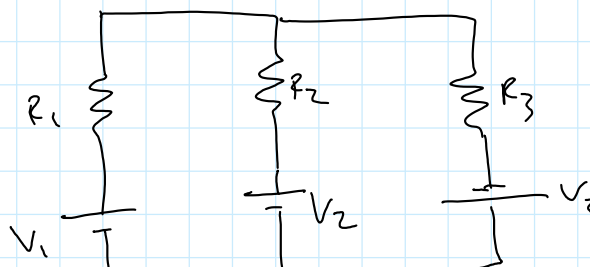

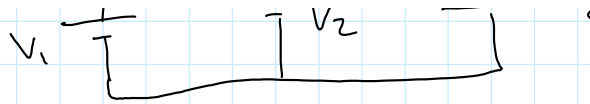


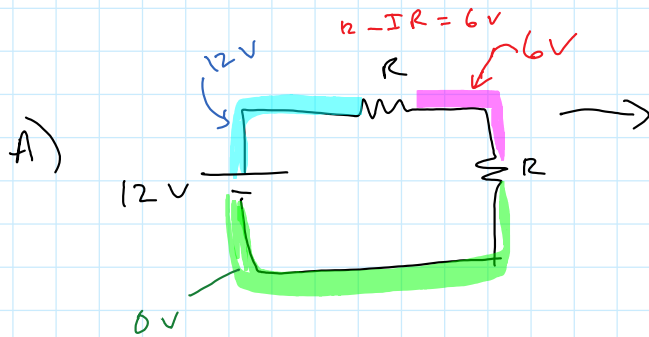Let $R = 12 \Omega$, find I for each circuit




$$12V \text{ --- } 24\Omega$$

$$I = \frac{V}{R} = 0.5 A$$

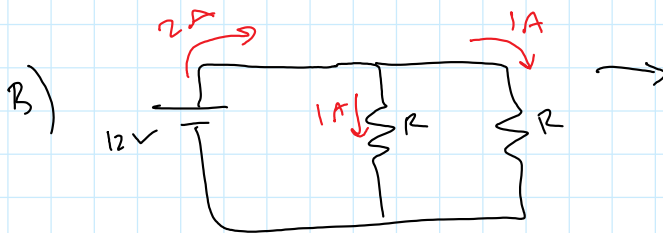


$$12V \text{ --- } 6\Omega$$

$$I = \frac{12V}{6\Omega} = 2 A$$

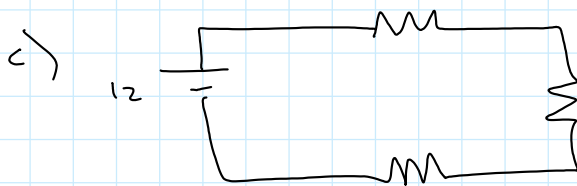

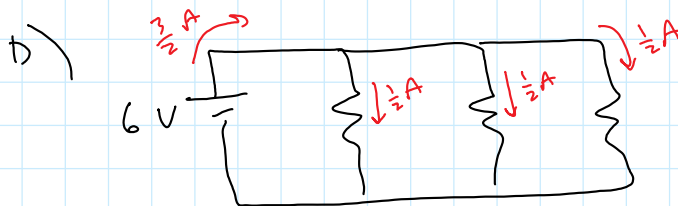
$$I = \frac{12V}{36\Omega} = \frac{1}{3} A$$



$$I_{\text{battery}} = \frac{3}{2} A$$

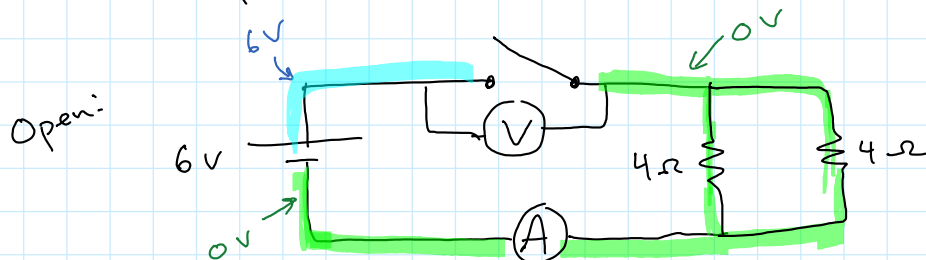
What do the meters read when the switches are open and/or closed?





	V	A
open	6	0
closed	0	3

closed:

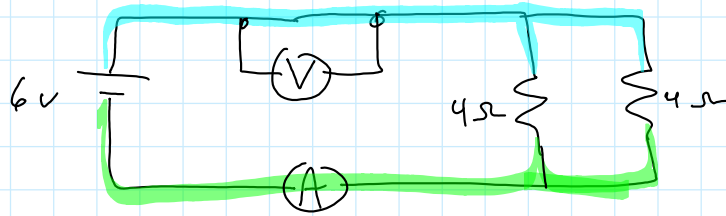

Ideal:

Voltmeter has infinite resistance

Ammeter has zero resistance