

**Last Lecture: Goals for the Lecture:**

- 1) Understand the terms current, drift velocity, and charge carrier
- 2) Understand Ohm's Law and how to find resistance of a conductor
- 3) Understand how temperature changes resistance in common conductive materials and in semiconductors and superconductors
- 4) Pay particular attention to equations: 27.1-27.3, 27.7-27.8, 27.10, 27.20, and 27.21-27.22
- 5) Be able to use series and parallel rules for resistor to solve circuit problems
- 6) Be able to use Kirchhoff's Rules to solve circuit problems

**Goals for the Lecture:**


- 1) Understand power dissipated in electrical devices and how to use it in solving problems
- 2) Understand EMF and internal resistance of batteries and power supplies
- 3) Understand RC circuits and their time constant,  $\tau$
- 4) Be able to do calculations involving time to charge and discharge capacitors in RC circuits

Battery and EMF :

Ideal:  $V_0 \frac{1}{\text{I}} = \text{Ideal battery or voltage source}$

No internal resistance  
 so, it always provides  
 the set voltage,  $V_0$ , no  
 matter the current flow

Real world:

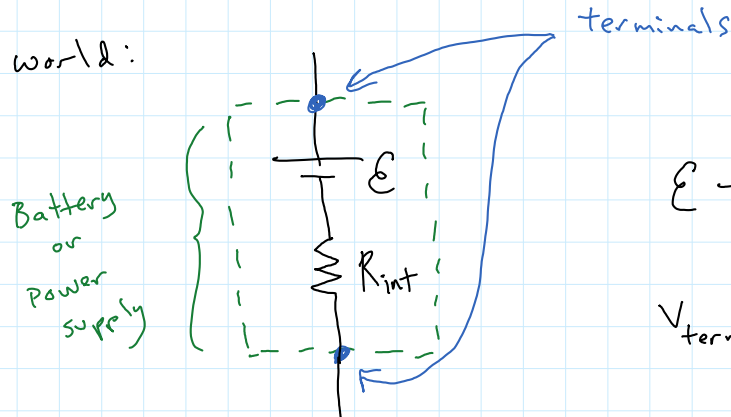

$\mathcal{E} \rightarrow \text{EMF}$   
 max voltage

$$V_{\text{terminal}} \leq \mathcal{E}$$

$$V_{\text{terminal}} = \mathcal{E} - I R_{\text{int}}$$

Worksheet  
 P. 99

$$\left. \begin{aligned}
 1) \quad V_A &= V_{\text{battery}} \\
 V_B &= \frac{1}{2} V_{\text{battery}} \\
 \dots & \dots
 \end{aligned} \right\}$$



$$V_A > V_B > V_C$$

$$V_B = \frac{1}{2} V_{\text{battery}}$$

$$V_C = \frac{1}{3} V_{\text{battery}}$$

$$V_A - V_B - C$$

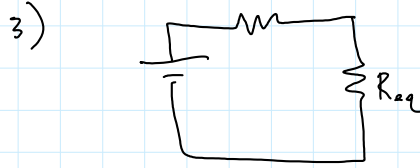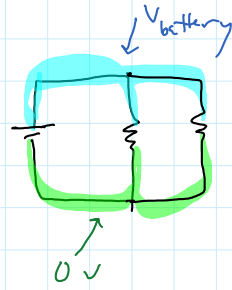2)  $V_A = V_B = V_C = V_{\text{battery}}$




$$(R_{eq})_A > (R_{eq})_B > (R_{eq})_C$$

$$V_C > V_B > V_A$$


↑  
largest  
current

D)  $V_A = V_B = V_{\text{battery}} > V_C = \frac{V_{\text{battery}}}{2}$


charging a capacitor:

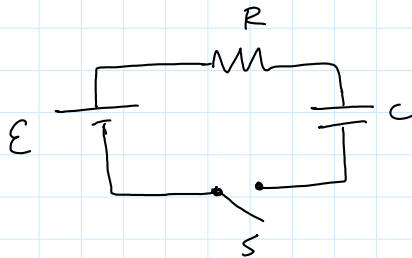

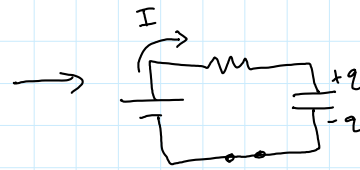Switch open  
No charge on Cap.  
No current



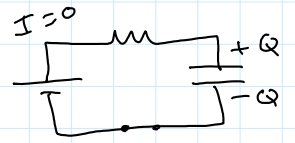Just after the  
switch is closed  
current flows  
cap. begins to charge



after a long  
time  
Cap. is fully  
charged  
No current  
flow

Loop rule:

$$E - IR - \frac{q}{C} = 0$$

q and I vary in time

$$I = \frac{dq}{dt}$$

$$I = \frac{dq}{dt}$$

$$I = \frac{\mathcal{E}}{R} - \frac{q}{RC}$$

$$\frac{dq}{dt} = \frac{\mathcal{E}}{R} - \frac{q}{RC} = - \frac{q - C\mathcal{E}}{RC}$$



$$\int \frac{dq}{q - C\mathcal{E}} = \int -\frac{1}{RC} dt$$

$$\ln \left( \frac{q - C\mathcal{E}}{-C\mathcal{E}} \right) = -\frac{t}{RC}$$

$$q(t) = Q \left( 1 - e^{-\frac{t}{RC}} \right)$$

$$I(t) = \frac{\mathcal{E}}{R} e^{-t/RC}$$

↑  
 $I_{\max}$

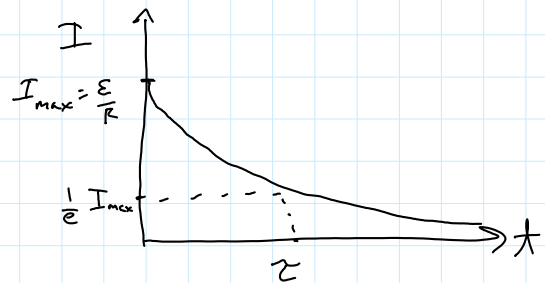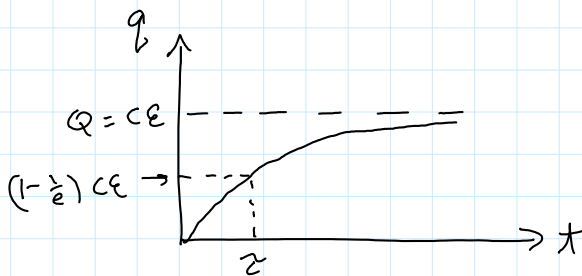


when  $t = RC$

$$q = \left( 1 - \frac{1}{e} \right) Q_{\max}$$

Time constant:  $\tau = RC$

Discharging:

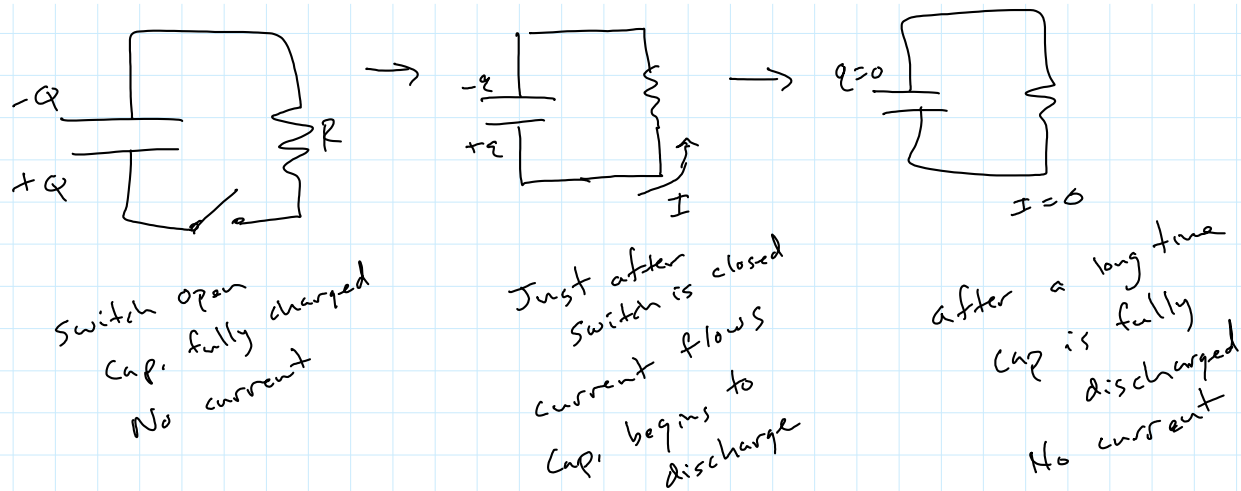

Loop Rule:

$$-\frac{q}{C} - IR = 0$$

$$I = \frac{dq}{dt}$$


$$q(t) = Q e^{-\frac{t}{RC}}$$

$$I(t) = -I_{\max} e^{-\frac{t}{RC}}$$


$$I_{\max} = \frac{Q}{RC}$$

↑  
indicates direction  
of discharging current  
is opposite the charging  
current

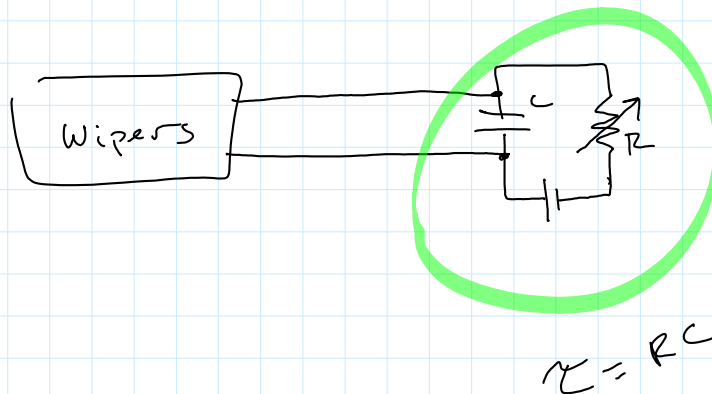Application: Intermittent Windshield Wipers




(V)

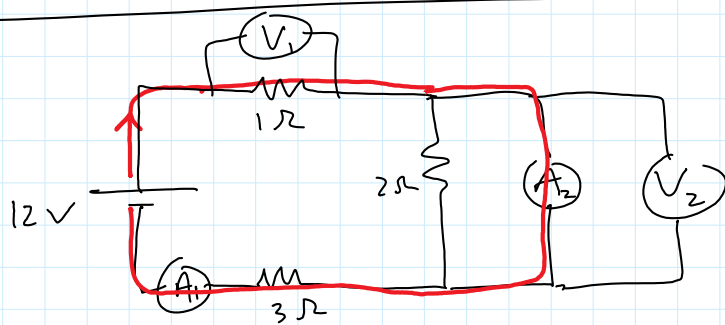

what does each ideal meter read:


$A_1$	3 A
$A_2$	3 A
$V_1$	3 V
$V_2$	0 V

2 Ω Resistor is shorted out

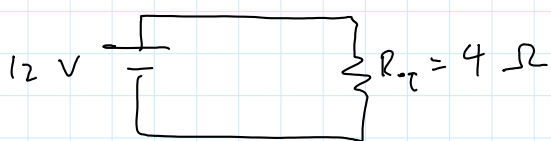


$$V = IR$$


$$I = \frac{12V}{4\Omega} = 3A$$

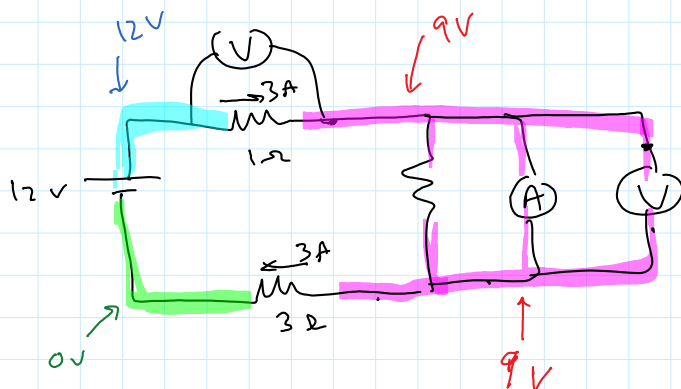


Ch 26 - 48

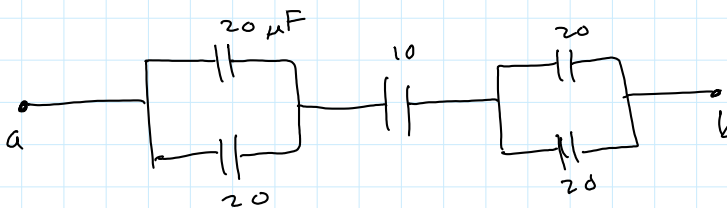

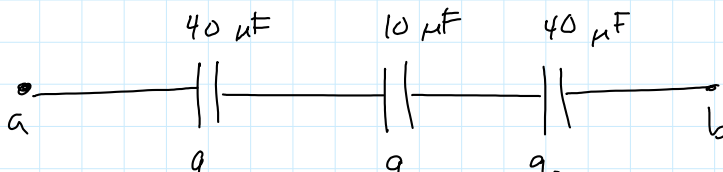If any one cap breaks down at 15 V  
find  $V_{ab}$  max for this configuration



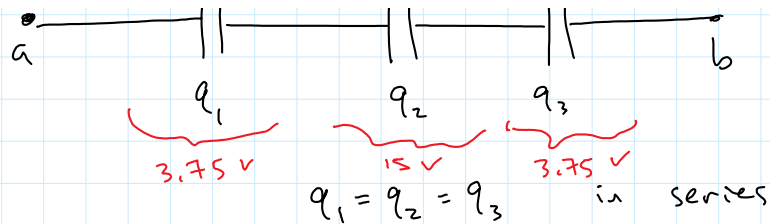

So,  $\Delta V_{10} > \Delta V_{40}$

10  $\mu\text{F}$  is first to break down

Let  $\Delta V_{10} = 15 \text{ V}$  and solve for  $\Delta V_{ab}$


$$Q = C V = (10 \mu\text{F}) (15 \text{ V}) = 150 \mu\text{C}$$

$$Q_{40} = 150 \mu\text{C} = (40 \mu\text{F}) (\Delta V_{40})$$


$$\Delta V_{40} = \frac{15}{4} = 3.75 \text{ V}$$

$$\begin{aligned} \Delta V_{ab} &= \Delta V_{40} + \Delta V_{10} + \Delta V_{40} \\ &= 22.5 \text{ V} \end{aligned}$$

ch. 28-24

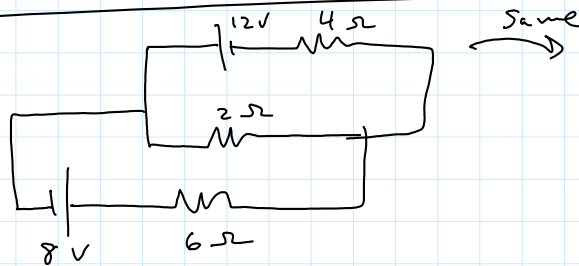

Find the current through each resistor

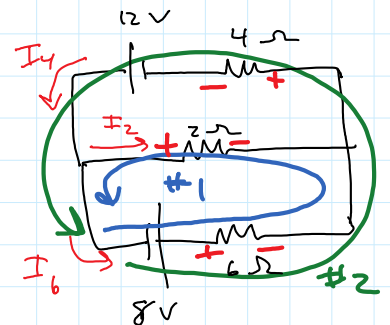

Junction:  $I_4 = I_2 + I_6$

Loop 1:  $8 \text{ V} - I_6(6) + I_2(2) = 0$


Loop 2:  $8 \text{ V} - I_6(6) - I_4(4) + 12 = 0$

$$I_2 = 909 \text{ mA}$$

$$I_6 = 1.64 \text{ A}$$

$$I_4 = 2.549 \text{ A}$$


Worksheet  
P. 107

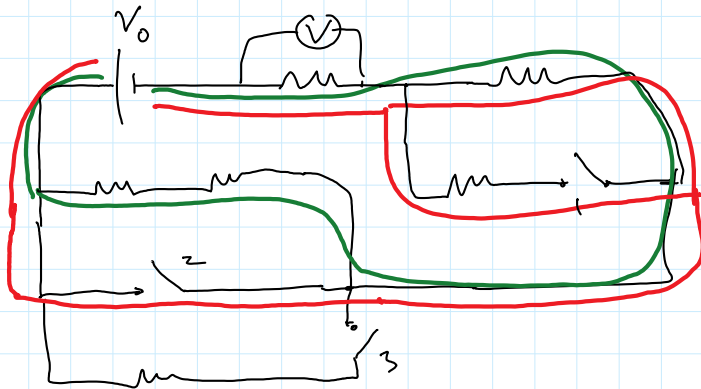


	$S_1$	$S_2$	$S_3$
A	open	open	open
G	closed	closed	open

A)  $V = \frac{1}{4} V_0$

G)

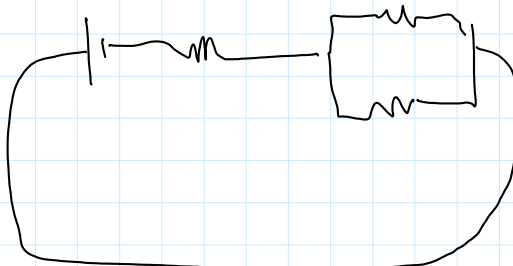

⇓

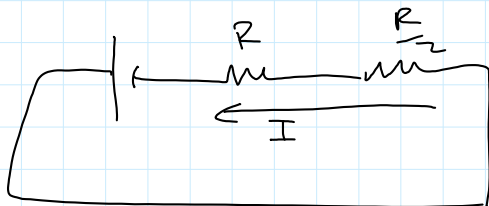

$$\begin{cases} V_R + V_{R/2} = V_0 \\ V_R = 2 V_{R/2} \end{cases}$$

$V = \frac{2}{3} V_0$