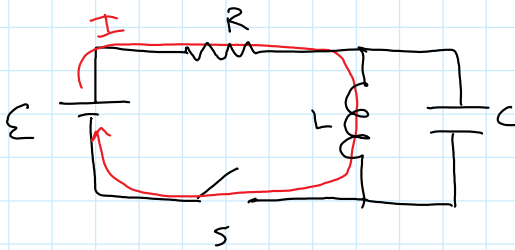


Goals for the Lecture:

- 1) Be able to calculate inductance and EMF generated across an inductor
- 2) Understand that RL circuits are very similar to RC circuits
- 3) Be able to solve problems involving time constants for RL circuits
- 4) Be able to calculate energy stored in the magnetic field of an inductor

Book Probs 32-47



switch is closed for a long time
after switch is opened -
 V_{\max} on Cap is 150V
What is L?

given:

$$E = 50 \text{ V}$$

$$R = 250 \Omega$$

$$C = 0.5 \mu\text{F}$$

at $t=0$:

$$\Delta V_L = 0 \rightarrow I_i = \frac{E}{R} = \frac{50}{250} = 0.2 \text{ A}$$

$$\Delta V_C = 0 \rightarrow Q_i = 0$$

$$U_{\text{total}} = U_L + U_C = \text{constant}$$

$$\frac{1}{2} L I^2 + \frac{1}{2} C V_c^2 = \text{constant}$$

$$U_{\text{total}} = \frac{1}{2} C (\Delta V_C)_{\max}^2 = \frac{1}{2} (0.5 \times 10^{-6} \text{ F}) (150 \text{ V})^2$$

$$= 5.625 \text{ mJ}$$

$$\frac{1}{2} L I_{\max}^2 = 5.625 \text{ mJ}$$

$$L = 2(5.625 \times 10^{-3}) = 0.01125 \text{ H}$$

$$L = \frac{2(5.025 \times 10^{-3})}{(0.2)^2} = 0.281 \text{ H}$$

AC Circuits


1) Resistors in AC circuits




AC Power Supply

$$V = V_{\max} \sin \omega t$$

$$V = I R$$

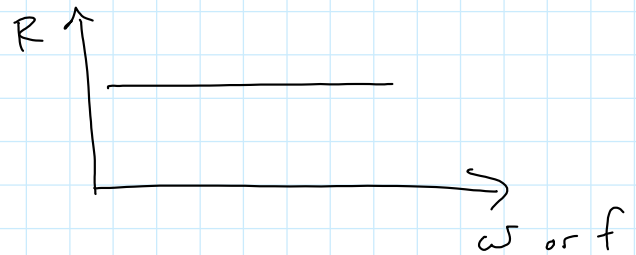


2) Inductors

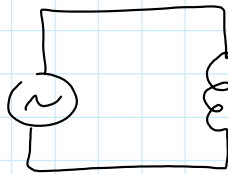


Reactance: X_L (Like Resistance)

$$V = I X_L$$

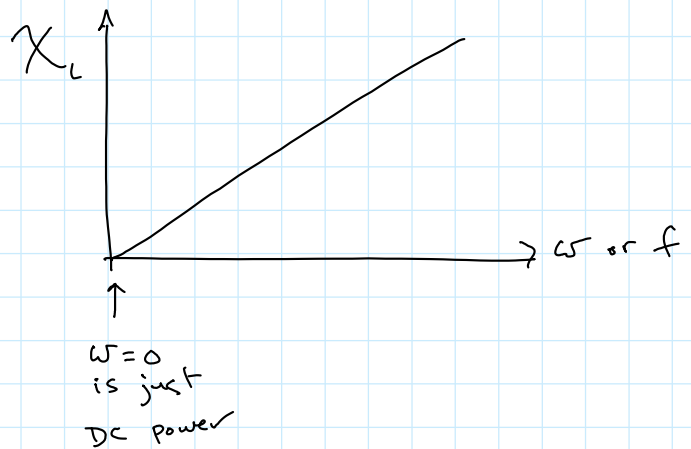


3) Capacitor

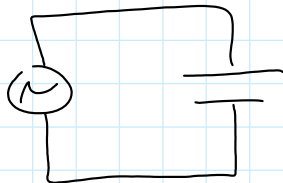

$$X_C = \frac{1}{\omega C}$$

$X_C \uparrow \uparrow$

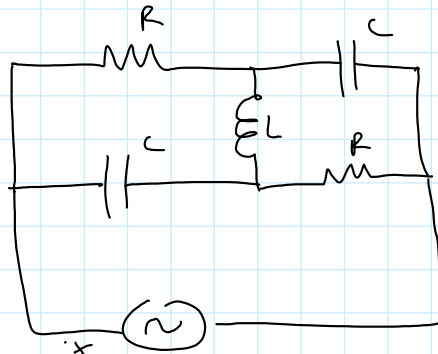

in high freq limit
 $f \rightarrow \infty$

in low freq limit
 $f \rightarrow 0$

$C \rightarrow$ zero resistance
 (a wire, a short)

$L \rightarrow$ infinite resistance
 (open circuit)

$C \rightarrow$ infinite Resistance
 (open)

$L \rightarrow$ zero resistance
 (a wire, short)

