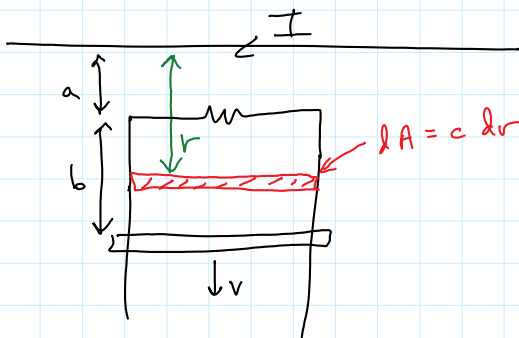


Goals for the Lecture:

- 1) Understand energy oscillations in LC circuits, including the natural frequency of the circuit, and be able to solve problems using energy conservation
- 2) Conceptually understand that RLC circuits are like damped harmonic oscillators
- 3) Understand that rms values are a type of "average" value used in AC circuit calculations and that, for sin and cos functions, the rms value is the maximum value divided by $\sqrt{2}$
- 4) Understand that capacitors and inductors can hinder the flow of electrons in a circuit and that we call this property reactance. Understand how the reactance changes with frequency for capacitors and inductors. Be able to solve circuit problems in the limit as the frequency goes to zero and as the frequency goes to infinity.
- 5) Understand transformers, the turns ratio, step up and step down transformers and be able to solve problems involving transformers.

From exam:



$$\mathcal{E} = \frac{d}{dt} \left[\int \vec{B} \cdot d\vec{A} \right] = \frac{d}{dt} \left[\int_a^{a+b} \frac{\mu_0 I}{2\pi r} c dr \right]$$

$$= \frac{d}{dt} \left[\frac{\mu_0 I c}{2\pi} \ln\left(\frac{a+b}{a}\right) \right]$$

both changing in time
so, chain rule

$$= \frac{\mu_0 c}{2\pi} \left[\frac{dI}{dt} \ln\left(\frac{a+b}{a}\right) + I \frac{d}{dt} \ln\left(\frac{a+b}{a}\right) \right]$$

$$= \frac{\mu_0 c}{2\pi} \left[4t \ln\left(\frac{a+b}{a}\right) + 0 \right]$$

$$= \frac{8}{\pi} \mu_0 c \ln\left(\frac{a+b}{a}\right)$$

$$\begin{aligned} \text{at } t=4\text{s} \\ I=0 \end{aligned}$$

$$I = 32 - 2t^2$$


$$I' = -4t$$

AC circuits


Power in a resistor:

$$p = i^2 R$$

↑ instantaneous current

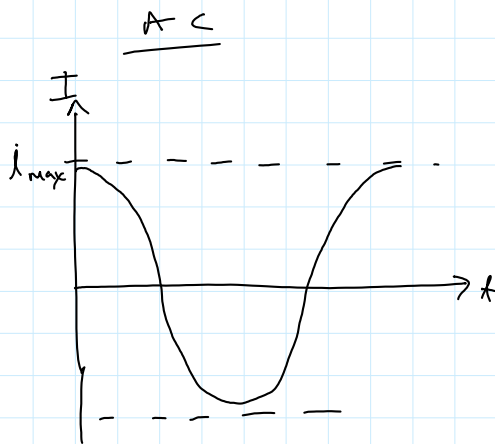

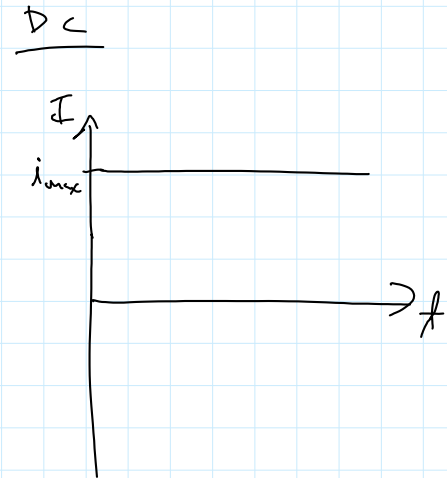much of the time
the current is
below i_{max}



current is always
at i_{max}

RMS - root-mean-square

$$I_{rms} = \sqrt{i^2}$$

For sin and cos:


$$I_{rms} = \frac{I_{max}}{\sqrt{2}}$$

$$P_{ave} = I_{rms}^2 R$$

$$V_{rms} = \frac{V_{max}}{\sqrt{2}}$$

$120 \text{ VAC} \rightarrow 120 \text{ V} = V_{\text{rms}}$
 $170 \text{ V} = V_{\text{max}}$

Resistor:

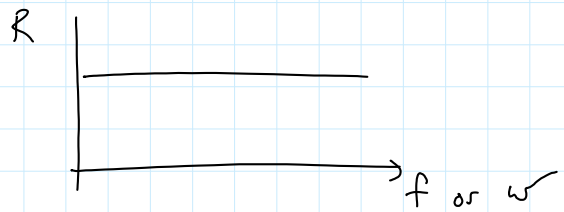

Inductor

$X_L = \omega L$




Capacitor

$X_C = \frac{1}{\omega C}$



RLC circuit

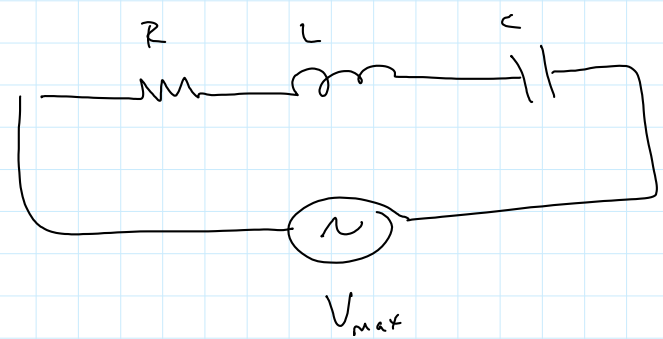


Impedance: $Z = \sqrt{R^2 + (X_L - X_C)^2}$

$$V_{\max} = I_{\max} Z$$

Resonance:

Circuit

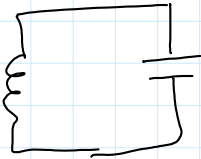

LC circuit


energy transferred
back and forth
between B & E fields

Analogy




frictionless harmonic oscillator

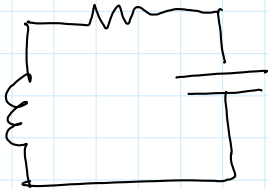
energy transferred back
and forth between
PE and KE



RLC circuit

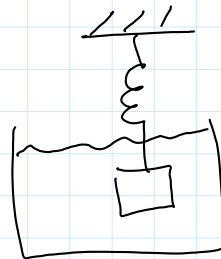

damped harmonic oscillator

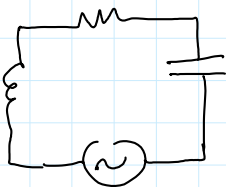


driven RLC
circuit




driven, damped
harmonic oscillator

If the EMF oscillates with the natural freq of the circuit ($\omega = \frac{1}{\sqrt{LC}}$) the circuit responds with a large current

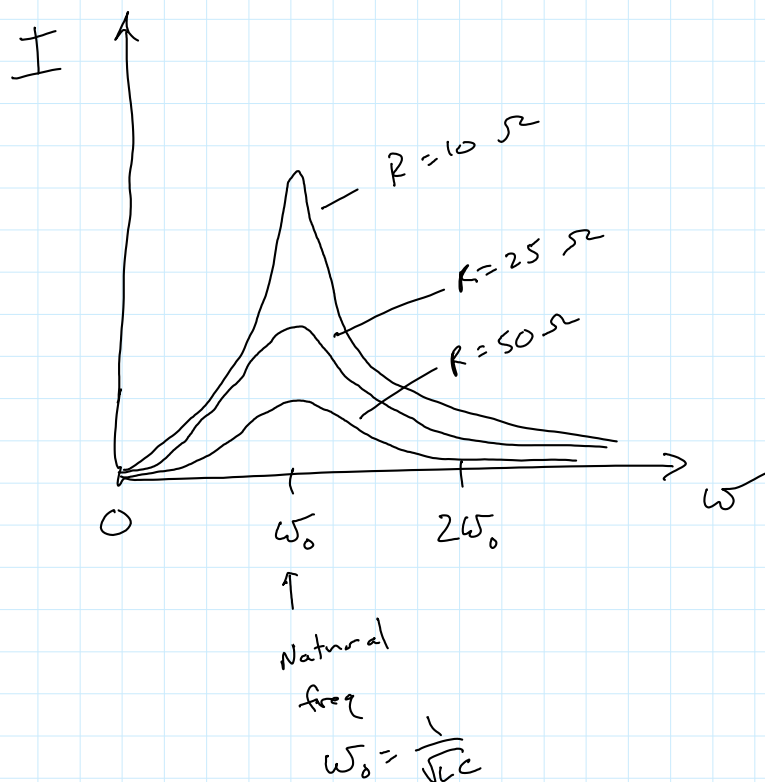Like pushing someone on a swing
 → if you push with the natural freq of the oscillator the Amplitude becomes large



Transformers:

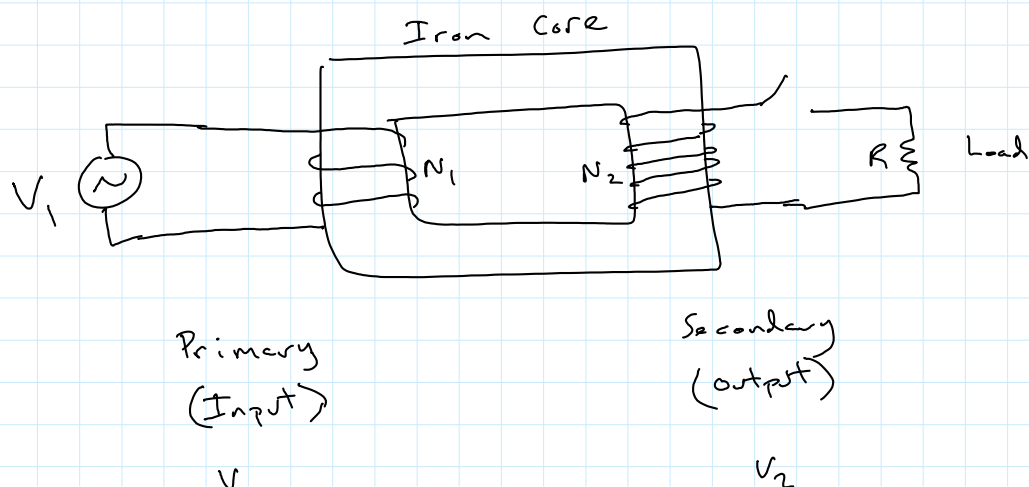

(INPUT)


$$V_1$$
$$N_1$$

✓

$$V_2$$
$$N_2$$

Ideal transformer: No energy loss

Real world: 90-99 %

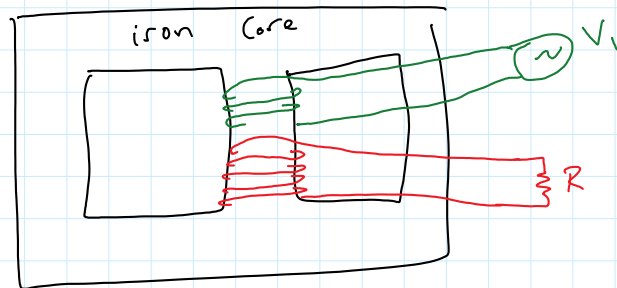

Let's look at Power:

$$P_1 = I_1 V_1 \quad \text{and} \quad P_2 = I_2 V_2$$

if ideal:

$$P_1 = P_2$$

$$I_1 V_1 = I_2 V_2$$

$$I_2 = \frac{V_1}{V_2} I_1 = \frac{N_1}{N_2} I_1$$

Since: $V_1 = -N_1 \frac{d\Phi_B}{dt}$

and $V_2 = -N_2 \frac{d\Phi_B}{dt}$

↑
Same for both

$$V_2 = \frac{N_2}{N_1} V_1$$

$$I_2 = \frac{N_1}{N_2} I_1$$

If Voltage goes up
 current goes down



$$P_1 = P_2$$

rectifier: converts AC to DC



Diode: Like a one-way valve for current




current can only flow this direction

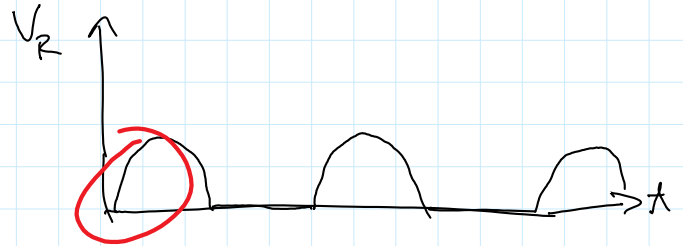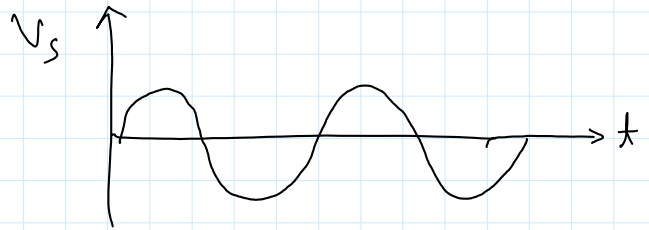

add a capacitor:

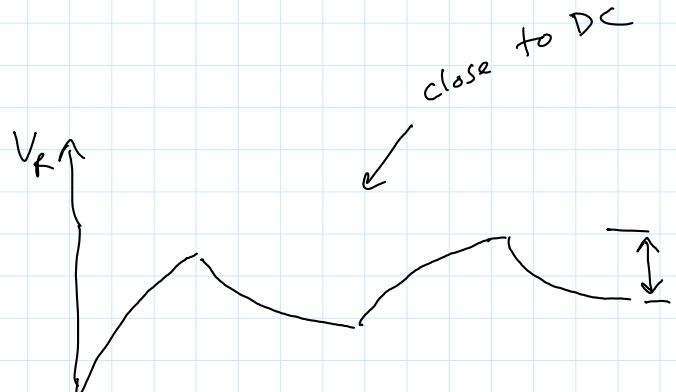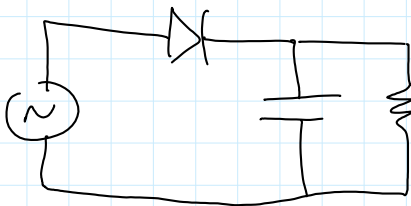


Include a transformer:

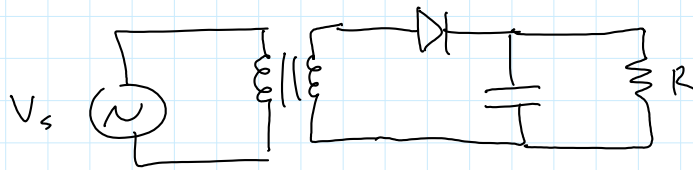


Supply
120 V
from wall
outlet

Step
down
transformer
to the
battery voltage
(maybe 9V)
but still AC

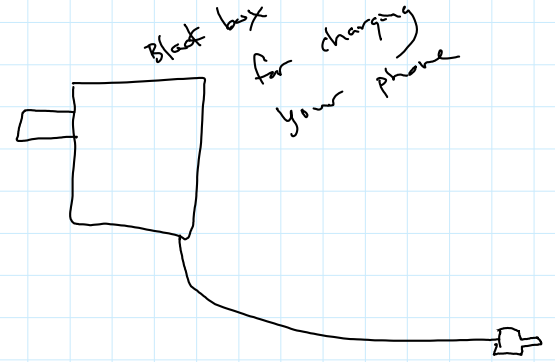
Approximate DC
at desired voltage
for your device




4 diodes are better:

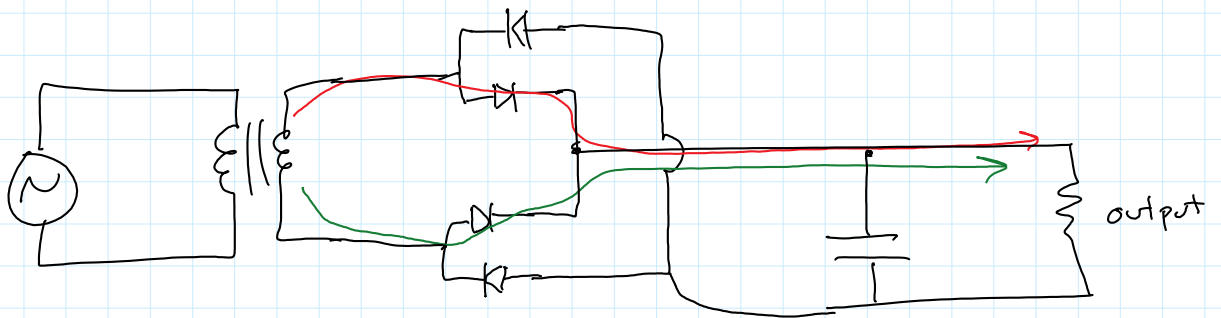

V_{cap}

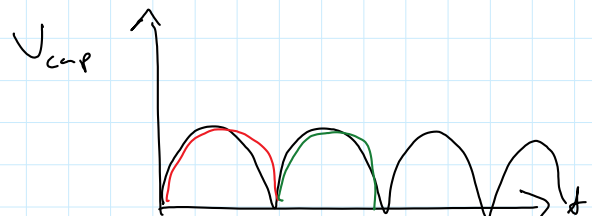


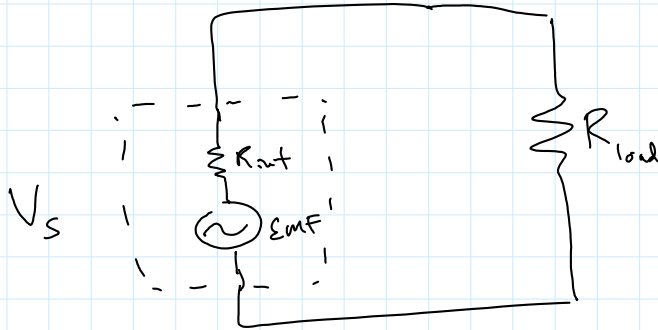

when $R_{int} = R_{load}$

you get maximum power delivered to load

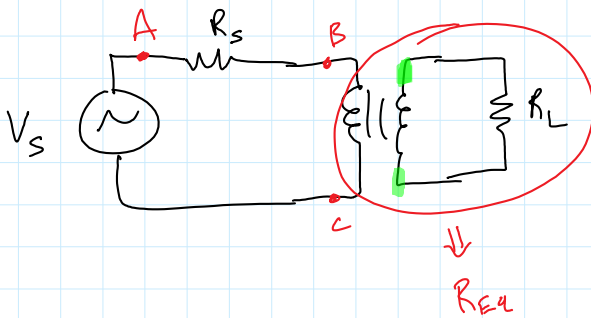by choosing appropriate turns ratio a transformer can be used to match the load resistance for max. power transfer:



$R_L = 50 \Omega$ (load resistance)

turns ratio: $N_1:N_2$ is 5:2

$V_s = 80 V_{rms}$

$V_L = 25 V_{rms}$


what is R_s ? source internal resistance

want current in primary \rightarrow use secondary current to find it:

$$V_L = I_2 R_L$$


$$I_2 = \frac{V_L}{R_L} = 0.5 \text{ A}$$
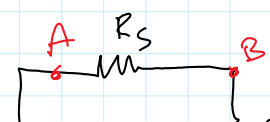
$$I_1 = \frac{N_2}{N_1} I_2 = 0.2 \text{ A}$$



voltage on primary of transformer
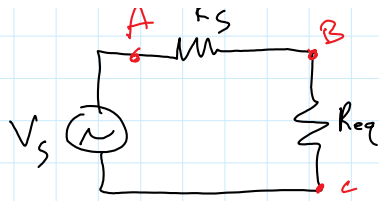
$$\Delta V_o = V_1 = \frac{N_1}{N_2} V_2 = 62.5 \text{ V}$$



$$\Delta V_{BC} = V_1 = \frac{N_1}{N_2} V_2 = 62.5 \text{ V}$$

$$V_s = V_{R_s} + V_{R_{eq}}$$

$$80 = I R_s + 62.5$$

$$R_s = \frac{17.5}{0.2} = 87.5 \text{ } \Omega$$

Maxwell's Equations:

$$\oint \vec{E} \cdot d\vec{A} = \frac{Q}{\epsilon_0}$$

Gauss's Law

→ charged particles create electric fields

$$\oint \vec{B} \cdot d\vec{A} = 0$$

Gauss's Law for magnetism

→ there are no magnetic monopoles

$$\oint \vec{E} \cdot d\vec{s} = - \frac{d\Phi_B}{dt}$$

Faraday's Law

→ a changing magnetic field creates an electric field

$$\oint \vec{B} \cdot d\vec{s} = \mu_0 I + \mu_0 \epsilon_0 \frac{d\Phi_E}{dt}$$

Ampere-Maxwell Law

1st part → currents create magnetic fields

2nd part → changing E fields create magnetic fields

we need one more:

$$\vec{F} = q (\vec{E} + \vec{v} \times \vec{B})$$


Lorentz Force Law

Classical Physics:

phy 4A { Newton's 1st Law
 " 2nd Law
 " 3rd Law
 " Law of gravity

phy 4B { Gauss's Law
 " " for mag.
 Faraday's Law
 Ampere - Maxwell Law
 Lorentz force Law

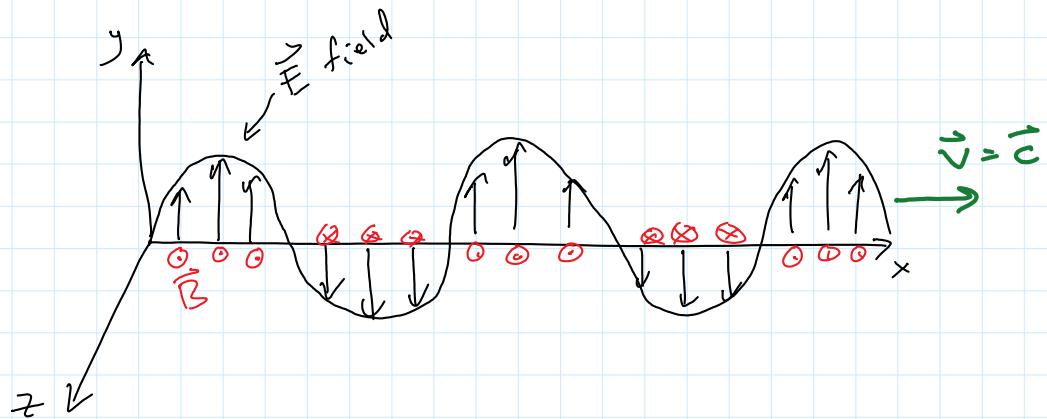phy 4C { 1st Law of thermodynamics
 2nd " " "





$$v = \frac{1}{\sqrt{\epsilon_0 \mu_0}} = 3.00 \times 10^8 \frac{m}{s} = c \quad \text{Speed of light}$$

Antenna:


E field signal



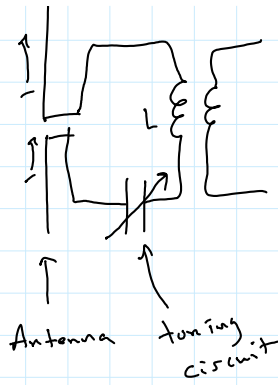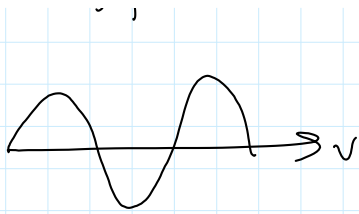Antenna acts like a little voltage source




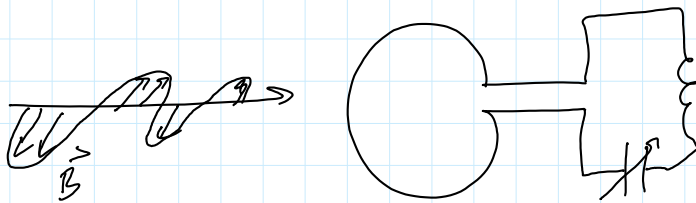Antenna acts like a little voltage source



changing B field

Electro-magnetic Spectrum:

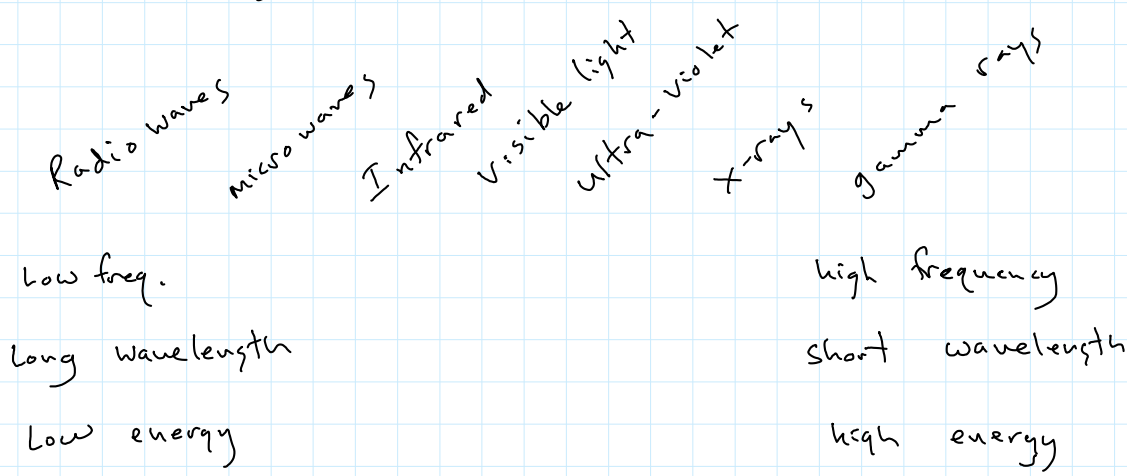


speed of a wave:

$$v = \lambda f$$

↑ wavelength ↑ frequency

Visible Light

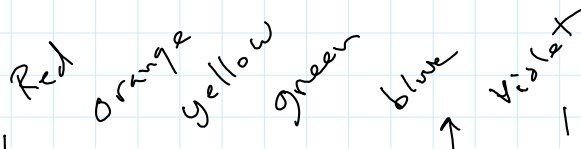

Red
|
 $\lambda = 700 \text{ nm}$

Orange
Yellow
Green
Blue
Indigo
Violet
|
400 nm