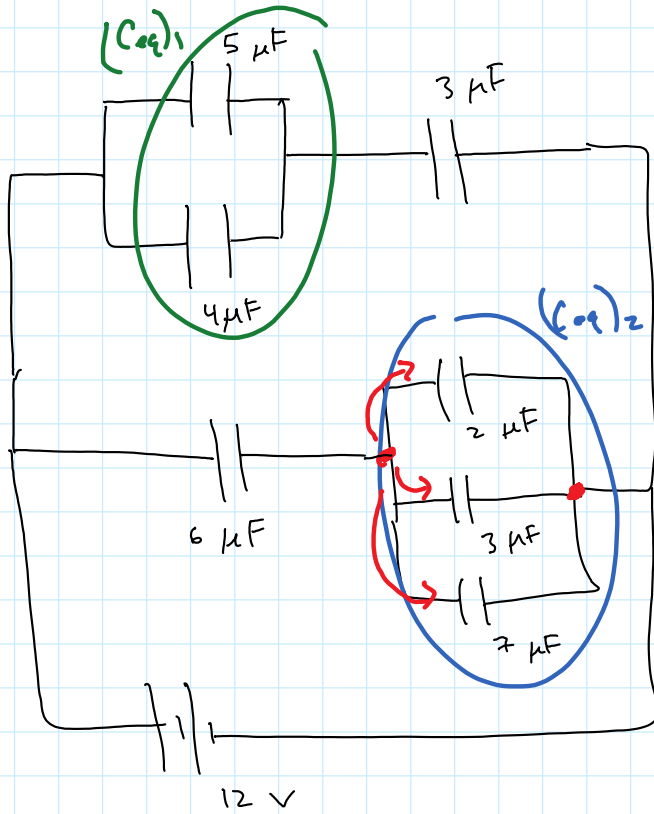


Book Problem 26-54
with a modification:


if $\Delta V_{\text{battery}} = 12 \text{ V}$

find the Q and ΔV for every capacitor



$$(C_{eq})_1 = 5 + 4 = 9 \mu\text{F}$$
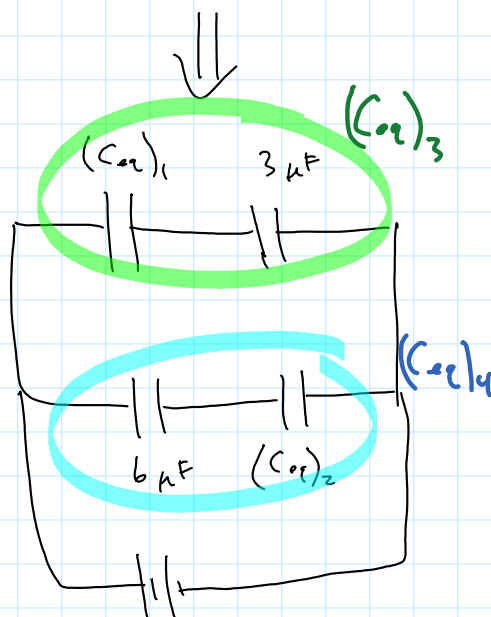
$$(C_{eq})_2 = 2 + 3 + 7 = 12 \mu\text{F}$$




$$\frac{1}{(C_{eq})_3} = \frac{1}{9} + \frac{1}{3} = \frac{4}{9}$$


$$(C_{eq})_3 = \frac{9}{4} \mu\text{F}$$

$$\frac{1}{(C_{eq})_4} = \frac{1}{6} + \frac{1}{12} = \frac{3}{12}$$

$$(C_{eq})_4 = 4 \mu\text{F}$$

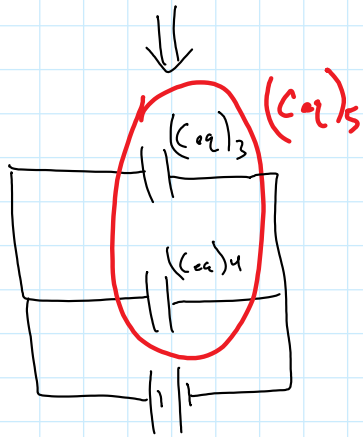

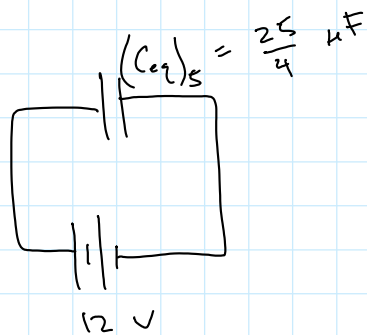
$$(C_{eq})_5 = \frac{9}{4} + 4 = \frac{25}{4}$$



$$Q = C V$$
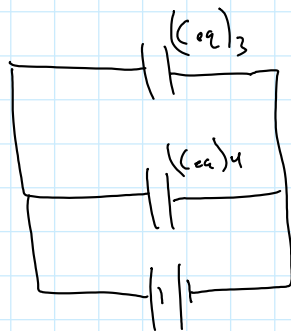
$$\begin{aligned} (Q_{eq})_5 &= (C_{eq})_5 (12) \\ &= \left(\frac{25}{4}\right) 12 \\ &= 75 \mu C \end{aligned}$$



$$\begin{aligned} (Q_{eq})_3 &= (C_{eq})_3 (12 \text{ V}) \\ &= \frac{9}{4} (12) = 27 \mu C \end{aligned}$$

$$\begin{aligned} (Q_{eq})_4 &= (C_{eq})_4 (12 \text{ V}) \\ &= 4 (12) = 48 \mu C \end{aligned}$$

check: $(Q_{eq})_3 + (Q_{eq})_4 = (Q_{eq})_5$

$$27 + 48 = 75$$

$$75 = 75 \quad \checkmark$$




$$Q_3 = 27 \mu\text{C}$$

$$\Delta V_3 = 9 \text{ V}$$

$$Q_6 = 48 \mu\text{C}$$

$$\Delta V_6 = 8 \text{ V}$$

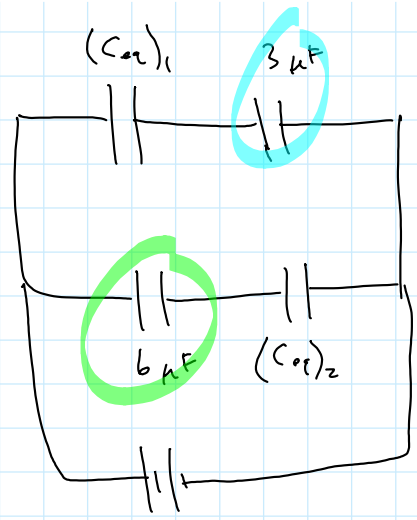

$$(Q_{eq})_1 = Q_3 = (Q_{eq})_3 = 27 \mu\text{C}$$

$$V_3 = \frac{Q_3}{C_3} = \frac{27}{3} = 9 \text{ V}$$

$$(V_{eq})_1 = \frac{27}{9} = 3 \text{ V}$$

$$(Q_{eq})_2 = Q_6 = (Q_{eq})_6 = 48 \mu\text{C}$$

$$V_6 = \frac{48}{6} = 8 \text{ V}$$

$$(V_{eq})_2 = \frac{48}{12} = 4 \text{ V}$$



$$Q_5 = 15 \mu\text{C}$$

$$\Delta V_5 = 3 \text{ V}$$

$$Q_4 = 12 \mu\text{C}$$

$$\Delta V_4 = 3 \text{ V}$$

$$Q_2 = 8 \mu\text{C}$$


$$\Delta V_2 = 4 \text{ V}$$

$$Q_3 = 12 \mu\text{C}$$

$$\Delta V_3 = 4 \text{ V}$$

$$Q_7 = 28 \mu\text{C}$$

$$\Delta V_7 = 4 \text{ V}$$

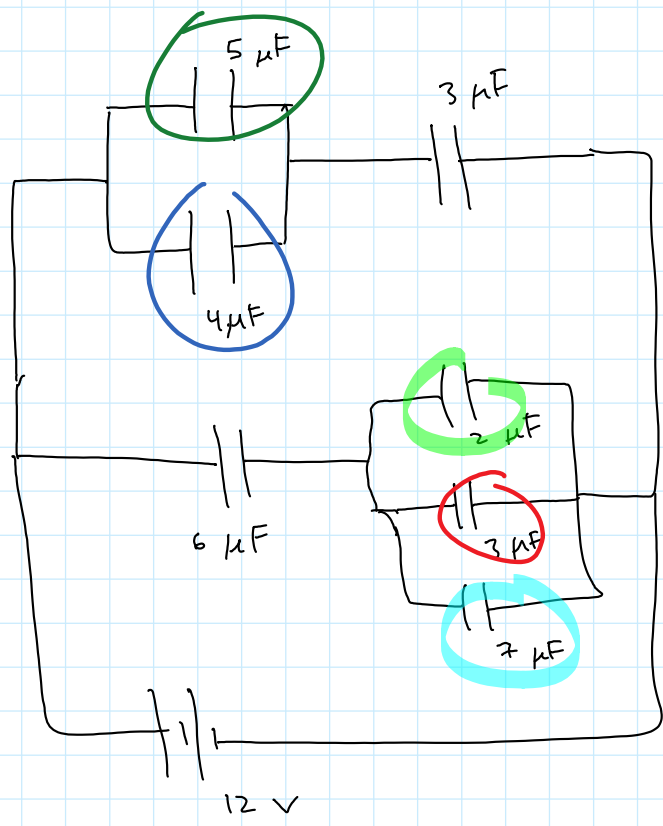

$$\Delta V_5 = \Delta V_4 = \Delta V_{(Ceq)1} = 3 \text{ V}$$

$$Q_4 = C_4(3) = 12 \mu\text{C}$$

$$Q_5 = C_5(3) = 15 \mu\text{C}$$

$$\text{check: } Q_4 + Q_5 = (Q_{eq})_1$$

$$27 = 27 \checkmark$$

$$\Delta V_2 = \Delta V_3 = \Delta V_7 = \Delta V_{(Ceq)2} = 4 \text{ V}$$

$$Q_2 = C_2(4) = 8 \mu\text{C}$$

$$Q_3 = C_3(4) = 12 \mu\text{C}$$

$$Q_7 = C_7(4) = 28 \mu\text{C}$$

$$\text{check: } Q_2 + Q_3 + Q_7 = (Q_{eq})_2$$

$$8 + 12 + 28 = 48$$

$$48 = 48 \checkmark$$